


Verilog assignment -1

Answers

 1. Build a circuit with no inputs and one output. That output should always drive 1 (or logic high).

Ans;


```
module top_module(  
    output reg one  
);  
    always @* begin  
        one = 1;  
    end  
endmodule
```



 2. Build a circuit with no inputs and one output that outputs a constant 0


Ans;

```
module top_module(  
    output zero  
);  
    assign zero=0;  
endmodule
```



 3. Create a module with one input and one output that behaves like a wire.

```
module top_module(  
    input in,  
    output out  
);  
    assign out = in;  
endmodule
```



4. Create a module with 3 inputs and 4 outputs that behaves like wires that makes these connections:

a -> w

b -> x

b -> y

c -> z

ans;

```
module top_module(
```

```
    input a, b, c,
```

```
    output w, x, y, z
```

```
);
```

```
    assign w = a;
```

```
    assign x = b;
```

```
    assign y = b;
```

```
    assign z = c;
```

```
endmodule
```



5. Create a module that implements a NOT gate.

Ans;

```
module top_module( input in, output out );
```

```
    assign out=~in;
```


```
endmodule
```

 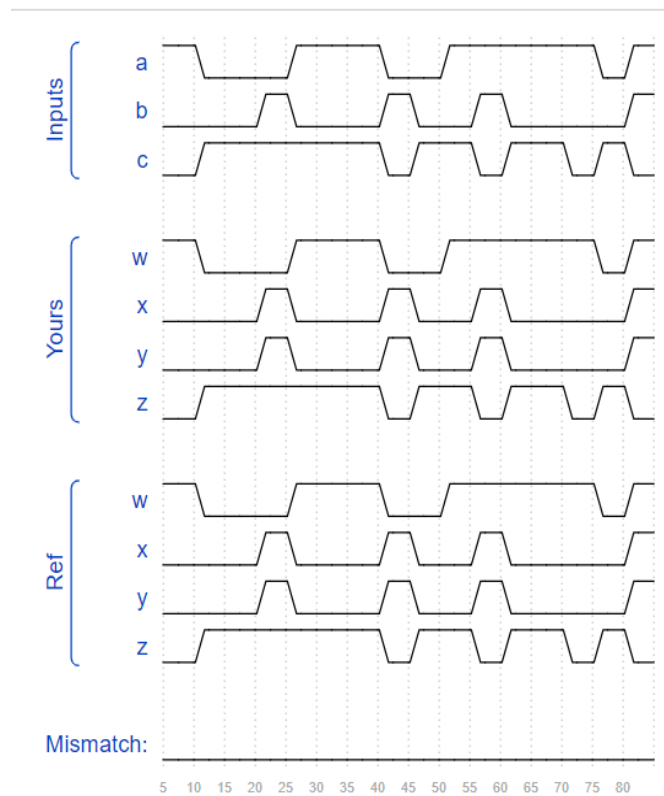

 6. Create a module that implements an AND gate.

Ans;


```
module top_module(
    input a,
    input b,
    output out );
    assign out=a&b;
endmodule
```



7. Create a module that implements a NOR gate. A NOR gate is an OR gate with its output inverted. A NOR function needs two operators when written in Verilog.

Ans;


```
module top_module(
    input a,
    input b,
    output out );
    assign out=~(a|b);
endmodule
```

 

 8. Create a module that implements an XNOR gate.


Ans;

```
module top_module(
    input a,
    input b,
    output out );
    assign out=~(a^b);
endmodule
```



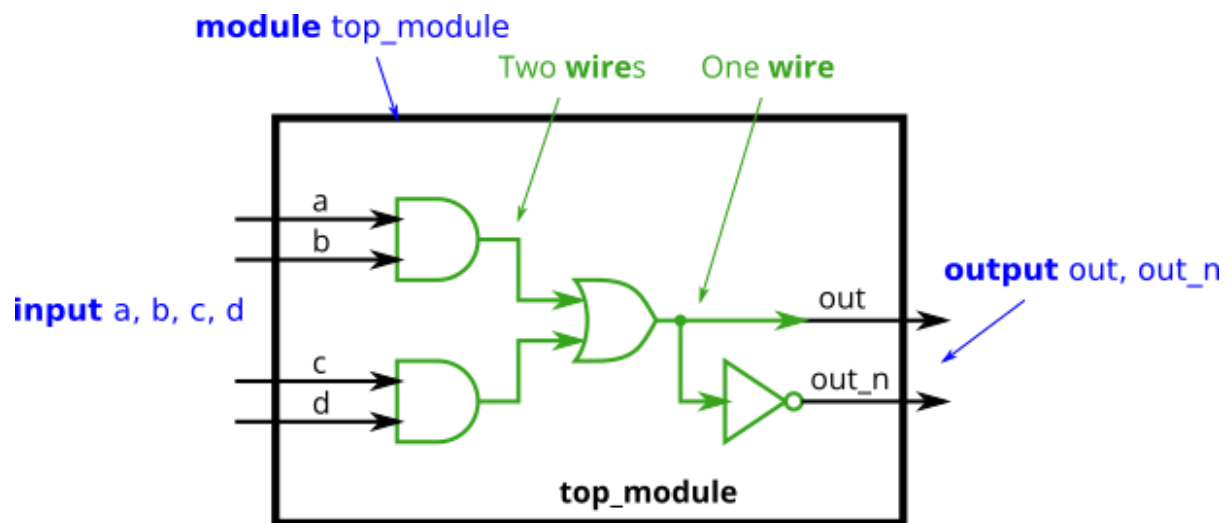9. Implement the following circuit. Create two intermediate wires (named anything you want) to connect the AND and OR gates together. Note that the wire that feeds the NOT gate is really wire out, so you do not necessarily need to declare a third wire here. Notice how wires are driven by exactly one source (output of a gate), but can feed multiple inputs.

If you're following the circuit structure in the diagram, you should end up with four assign statements, as there are four signals that need a value assigned.



Ans;

```
`default_nettype none
```

```
module top_module(
```

```
    input a,
```

```
    input b,
```

```
    input c,
```

```
    input d,
```

```
    output out,
```

```
    output out_n );
```

```
wire x,y;
```


```
    assign x=a&b;
```

```
    assign y=c&d;
```

```
    assign out=x|y;
```

```
    assign out_n=~out;
```

```
endmodule
```

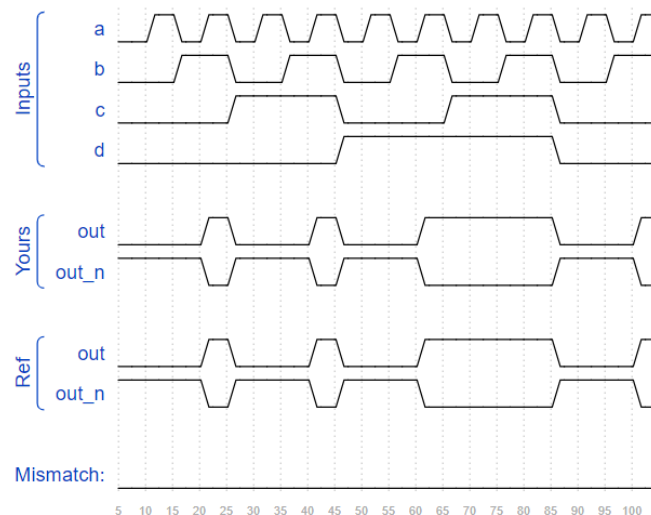


10. The 7458 is a chip with four AND gates and two OR gates. This problem is slightly more complex than 7420.

Ans;


```

module top_module (
    input p1a, p1b, p1c, p1d, p1e, p1f,
    output p1y,
    input p2a, p2b, p2c, p2d,
    output p2y );
wire w1,w2,w3,w4;
    and(w1,p1a,p1b,p1c);
    and(w2,p1d,p1e,p1f);
    or(p1y,w1,w2);
    and(w3,p2a,p2b);
    and(w4,p2c,p2d);
    or(p2y,w3,w4);
endmodule

```

 

11.

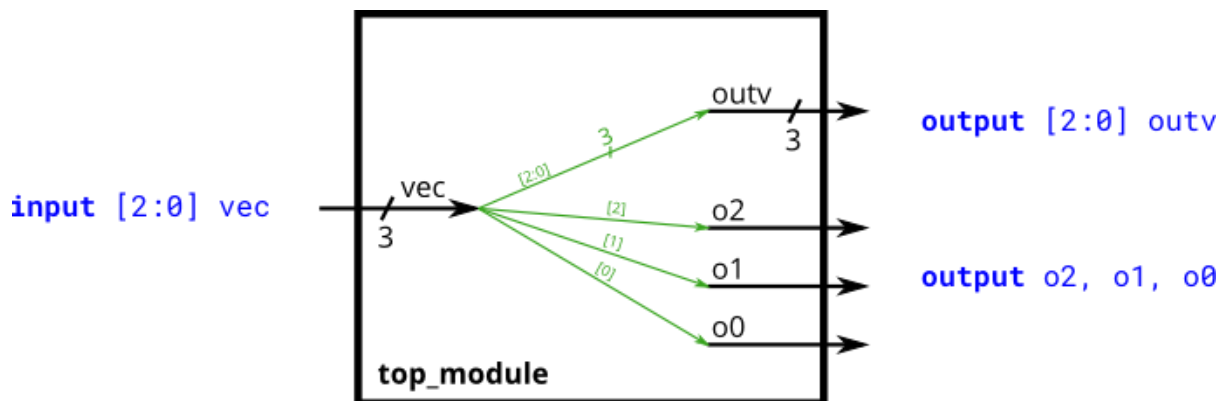


Ans;

```

module top_module (
    input wire [2:0] vec,
    output wire [2:0] outv,
    output wire o2,
    output wire o1,
    output wire o0 );

```

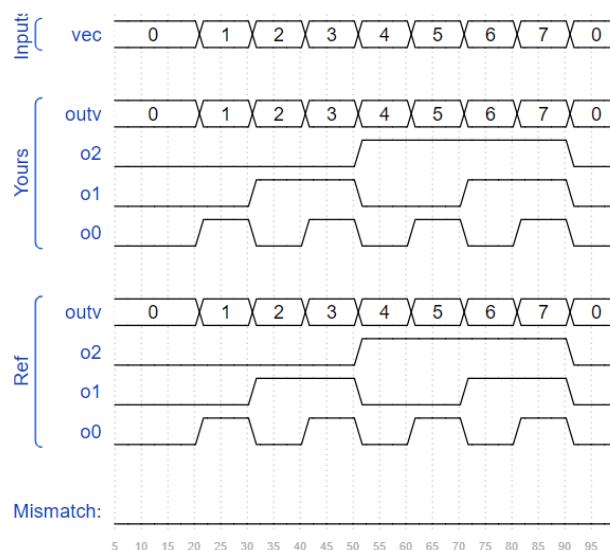

```

assign outv = vec;

assign o0 = vec[0];

assign o1 = vec[1];

assign o2 = vec[2];

```

endmodule

12. Build a combinational circuit that splits an input half-word (16 bits, [15:0]) into lower [7:0] and upper [15:8] bytes.


Ans;

```

module top_module(
    input wire [15:0] in,
    output wire [7:0] out_hi,
    output wire [7:0] out_lo );
    assign out_hi = in[15:8];
    assign out_lo = in[7:0];

```

endmodule

 

13. A 32-bit vector can be viewed as containing 4 bytes (bits [31:24], [23:16], etc.). Build a circuit that will reverse the byte ordering of the 4-byte word.

AaaaaaaaaBbbbbbbbCcccccccDddddddd => DdddddddCcccccccBbbbbbbbAaaaaaaaa


Ans;

```

module top_module(
    input [31:0] in,
    output [31:0] out );
    assign out[7:0] = in[31:24];
    assign out[15:8] = in[23:16];
    assign out[23:16] = in[15:8];
    assign out[31:24] = in[7:0];

```


endmodule

 

14. Build a circuit that has two 3-bit inputs that computes the bitwise-OR of the two vectors, the logical-OR of the two vectors, and the inverse (NOT) of both vectors. Place the inverse of b in the upper half of out_not (i.e., bits [5:3]), and the inverse of a in the lower half.

Ans;

```
module top_module(
    input [2:0] a,
    input [2:0] b,
    output [2:0] out_or_bitwise,
    output out_or_logical,
    output [5:0] out_not
);
    assign out_or_bitwise = a | b;
    assign out_or_logical = a || b;
    assign out_not[5:3] = ~b;
    assign out_not[2:0] = ~a;
endmodule
```

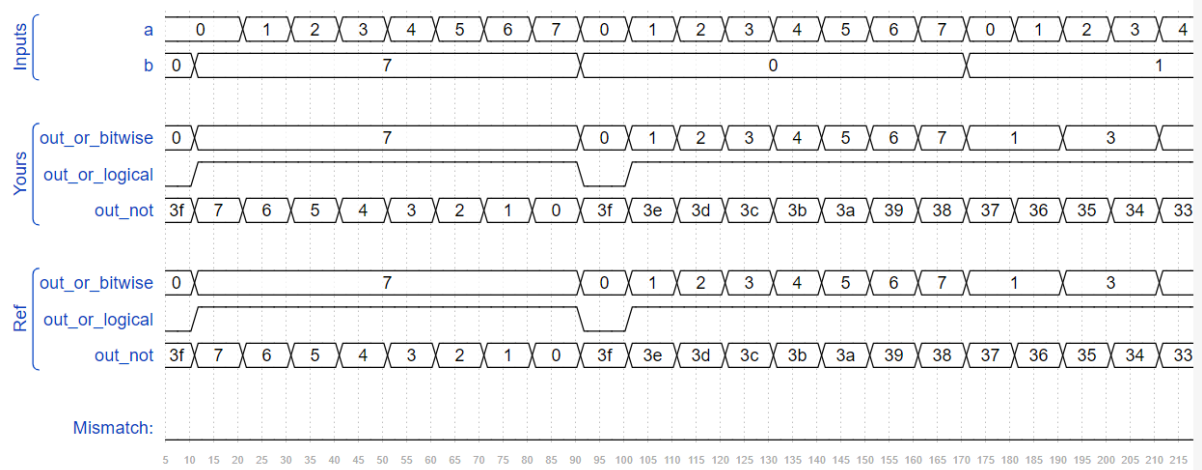

15. Build a circuit that has two 3-bit inputs that computes the bitwise-OR of the two vectors, the logical-OR of the two vectors, and the inverse (NOT) of both vectors. Place the inverse of *b* in the upper half of *out_not* (i.e., bits [5:3]), and the inverse of *a* in the lower half.

Ans;

```
module top_module(
    input [2:0] a,
    input [2:0] b,
    output [2:0] out_or_bitwise,
    output out_or_logical,
```

```

output [5:0] out_not);

assign out_or_bitwise = a | b;


assign out_or_logical = a || b;

assign out_not[5:3] = ~b;

assign out_not[2:0] = ~a;

```

endmodule

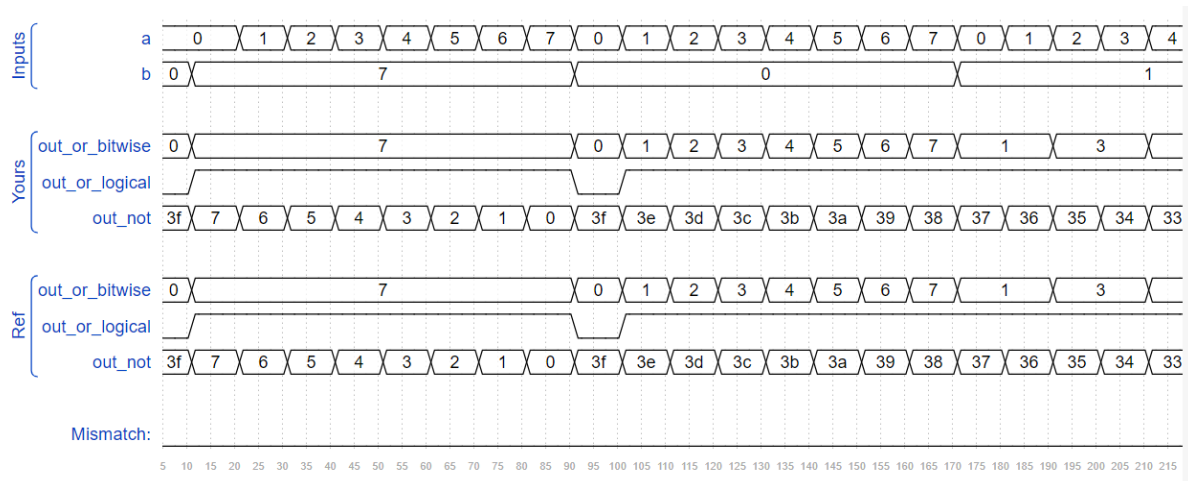

16. Build a combinational circuit with four inputs, in[3:0].

There are 3 outputs:

out_and: output of a 4-input AND gate.

out_or: output of a 4-input OR gate.

out_xor: output of a 4-input XOR gate.

Ans;

```

module top_module(

```

```

    input [3:0] in,

```

```

    output out_and,

```

```

    output out_or,

```

```

    output out_xor

```

```

);

```

```

    assign out_and = in[3] && in[2] && in[1] && in[0];

```

```

    assign out_or = in[3] || in[2] || in[1] || in[0];

```

```


    assign out_xor = in[3] ^ in[2] ^ in[1] ^ in[0];

```

```

endmodule


```

 

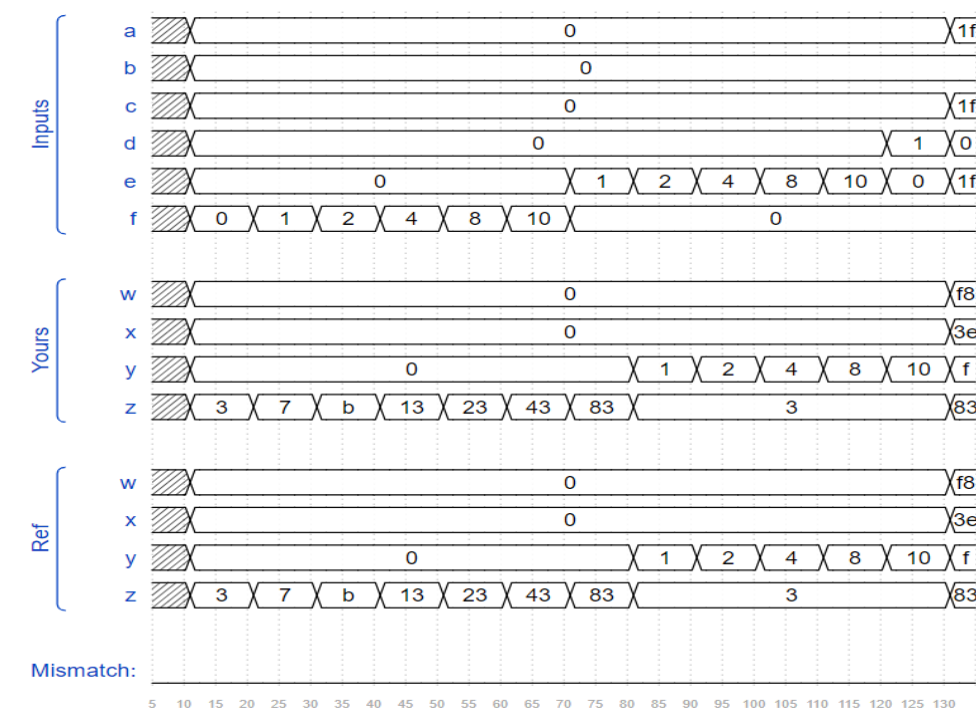17. Given several input vectors, concatenate them together then split them up into several output vectors. There are six 5-bit input vectors: a, b, c, d, e, and f, for a total of 30 bits of input. There are four 8-bit output vectors: w, x, y, and z, for 32 bits of output. The output should be a concatenation of the input vectors followed by two 1 bits:

Ans;

```
module top_module (
    input [4:0] a, b, c, d, e, f,
    output [7:0] w, x, y, z );
    wire [31:0] concat_reg;
    assign concat_reg = {a[4:0], b[4:0], c[4:0], d[4:0], e[4:0], f[4:0], 2'b11};
    assign w = concat_reg[31:24];
    assign x = concat_reg[23:16];
    assign y = concat_reg[15:8];
    assign z = concat_reg[7:0];
endmodule
```




18. Given an 8-bit input vector [7:0], reverse its bit ordering.

Ans;

```
module top_module(
    input [7:0] in,
    output [7:0] out
);
```

```
    assign out = {in[0],in[1],in[2],in[3],in[4],in[5],in[6],in[7]};
```

```
endmodule
```

 

19. Build a circuit that sign-extends an 8-bit number to 32 bits. This requires a concatenation of 24 copies of the sign bit (i.e., replicate bit[7] 24 times) followed by the 8-bit number itself.

Ans;

```
module top_module (
    input [7:0] in,
    output [31:0] out );
```

```
    assign out = { {24{in[7]}} , in[7:0] };
```

```
endmodule
```

20. Given five 1-bit signals (a, b, c, d, and e), compute all 25 pairwise one-bit comparisons in the 25-bit output vector. The output should be 1 if the two bits being compared are equal.

out[24] = ~a ^ a; // a == a, so out[24] is always 1.


out[23] = ~a ^ b;

out[22] = ~a ^ c;

...

out[1] = ~e ^ d;

out[0] = ~e ^ e;

 

Vector5.png

As the diagram shows, this can be done more easily using the replication and concatenation operators.


The top vector is a concatenation of 5 repeats of each input

The bottom vector is 5 repeats of a concatenation of the 5 inputs

Ans;


```
module top_module (
    input a, b, c, d, e,
    output [24:0] out );//
    assign out = ~{ {5{a}}, {5{b}}, {5{c}}, {5{d}}, {5{e}} } ^ { {5{a,b,c,d,e}} };
endmodule
```

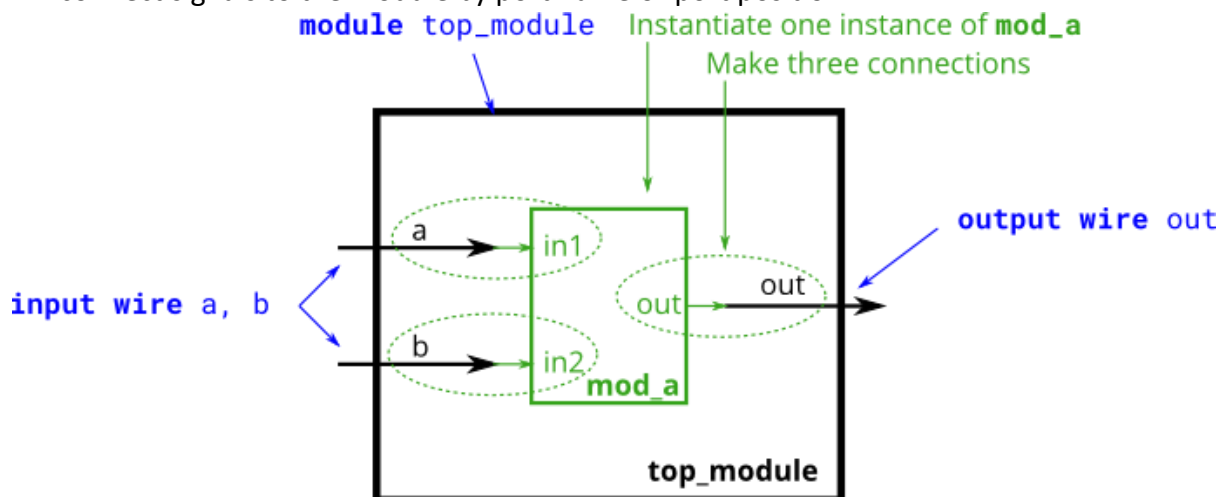21. connect signals to the module by port name or port position.




Ans;
 
```
module top_module ( input a, input b, output out );
    mod_a instance_1(a,b,out);
endmodule
```



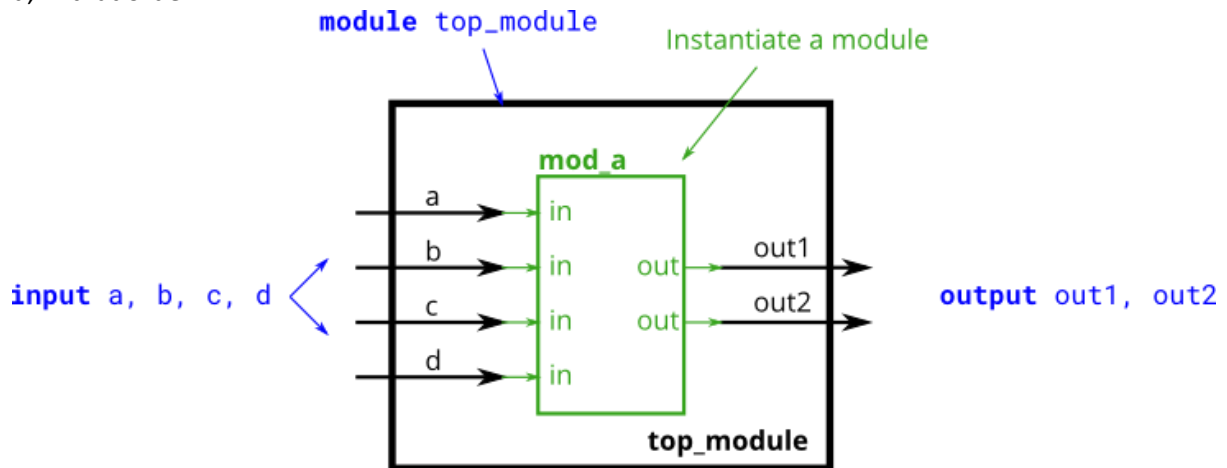22. You must connect the 6 ports by position to your top-level module's ports out1, out2, a, b, c, and d, in that order.



Ans;

```
module top_module (
```

```
    input a,
```

```
    input b,
```

```
    input c,
```

```
    input d,
```


```
    output out1,
```

```
    output out2
```


```
);
```

```
    mod_a inst_1(out1,out2,a,b,c,d);
```

```
endmodule
```

 


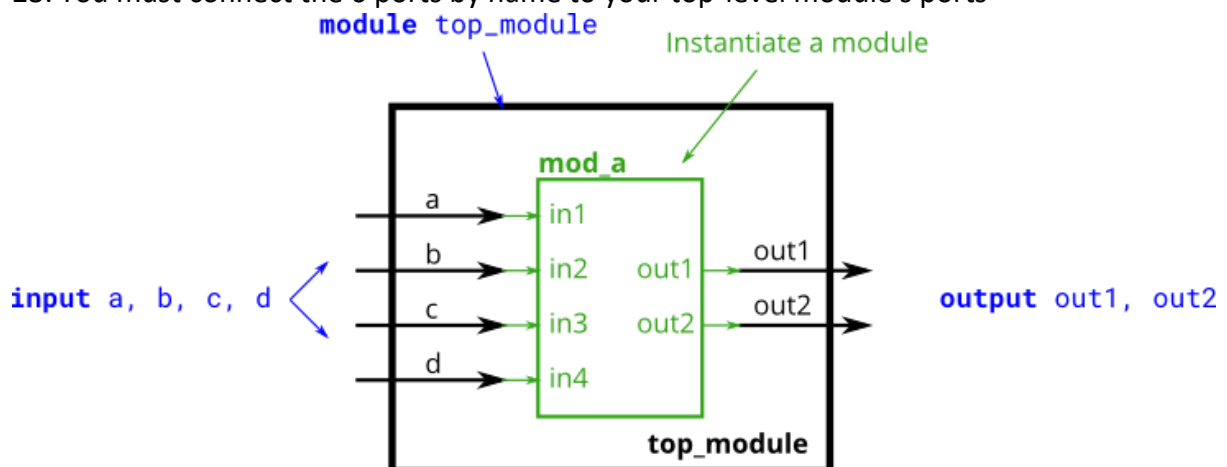23. You must connect the 6 ports by name to your top-level module's ports



Ans;

 
```
module top_module (
    input a,
    input b,
    input c,
    input d,
    output out1,
    output out2
);
```



```
    mod_a inst_1(.in1(a),.in2(b),.in3(c),.in4(d),.out1(out1),.out2(out2));
```


```
endmodule
```

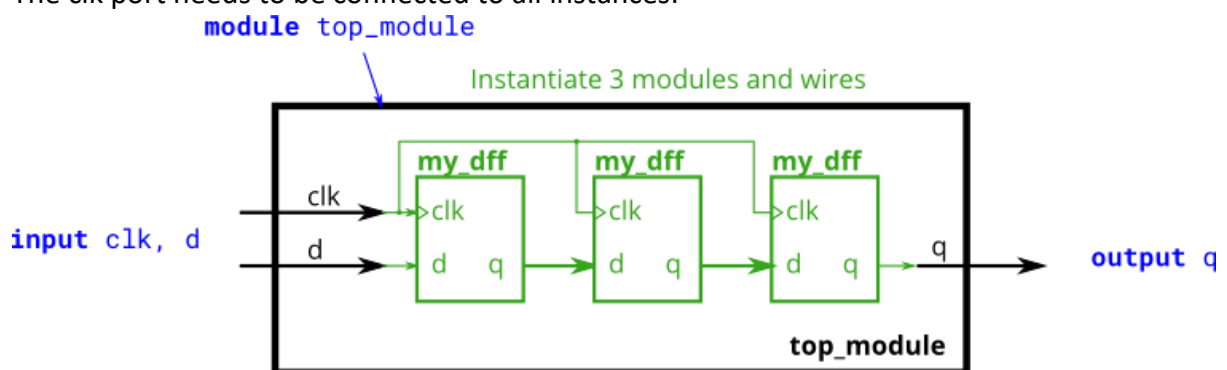24. Instantiate three of them, then chain them together to make a shift register of length 3. The clk port needs to be connected to all instances.




Ans;
 
```
module top_module ( input clk, input d, output q );
    wire con1,con2;
    my_dff d_flop1(.clk(clk),.d(d),.q(con1));
    my_dff d_flop2(.clk(clk),.d(con1),.q(con2));
    my_dff d_flop3(.clk(clk),.d(con2),.q(q));
endmodule
```



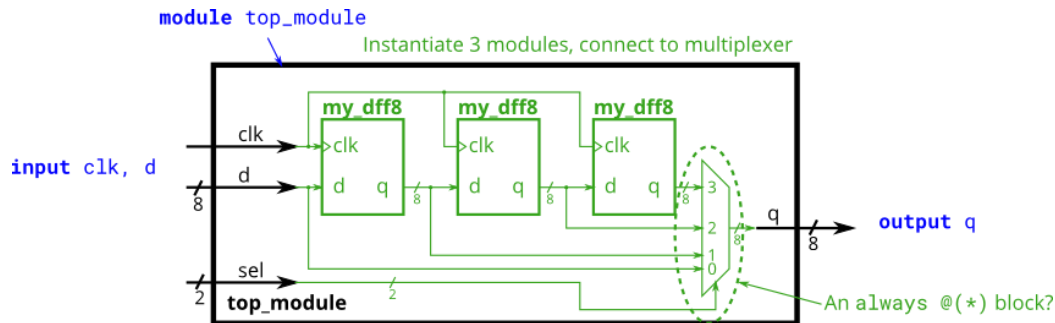25. You are given a module `my_dff8` with two inputs and one output (that implements a set of 8 D flip-flops). Instantiate three of them, then chain them together to make a 8-bit wide shift register of length 3. In addition, create a 4-to-1 multiplexer (not provided) that chooses what to output depending on `sel[1:0]`: The value at the input `d`, after the first, after the second, or after the third D flip-flop. (Essentially, `sel` selects how many cycles to delay the input, from zero to three clock cycles.)



Ans;

module top_module (

input clk,

input [7:0] d,

input [1:0] sel,

output reg [7:0] q

);

wire [7:0] con1, con2, con3;

my_dff8 d_flop1(.clk(clk), .d(d), .q(con1));

my_dff8 d_flop2(.clk(clk), .d(con1), .q(con2));

my_dff8 d_flop3(.clk(clk), .d(con2), .q(con3));

always @ (*) begin

case(sel)

0 : q = d ;

1 : q = con1;


2 : q = con2;

3 : q = con3;

endcase


end

endmodule

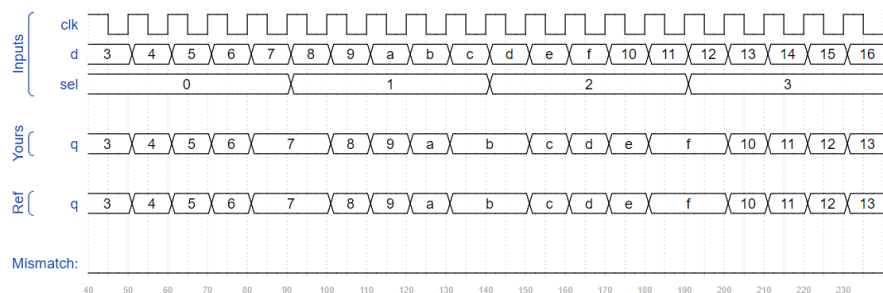

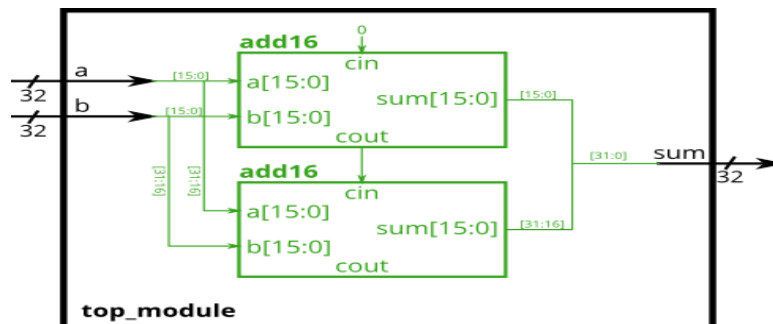26. You are given a module add16 that performs a 16-bit addition. Instantiate two of them to create a 32-bit adder. One add16 module computes the lower 16 bits of the addition result, while the second add16 module computes the upper 16 bits of the result, after receiving the carry-out from the first adder. Your 32-bit adder does not need to handle carry-in (assume 0) or carry-out (ignored), but the internal modules need to in order to function correctly. (In other words, the add16 module performs 16-bit $a + b + \text{cin}$, while your module performs 32-bit $a + b$).

Connect the modules together as shown in the diagram below. The provided module add16 has the following declaration:



Ans;


```
module top_module(
    input [31:0] a,
    input [31:0] b,
    output [31:0] sum
);
```

```
    wire con1, con2;
```

```
    add16 adder_1(a[15:0], b[15:0], 0, sum[15:0], con1);
```

```
    add16 adder_2(a[31:16], b[31:16], con1, sum[31:16], con2);
```

```
endmodule
```

 

27. you are given a module add16 that performs a 16-bit addition. You must instantiate two of them to create a 32-bit adder. One add16 module computes the lower 16 bits of the addition result, while the second add16 module computes the upper 16 bits of the result. Your 32-bit adder does not need to handle carry-in (assume 0) or carry-out (ignored).

Connect the add16 modules together as shown in the diagram below. The provided module add16 has the following declaration:

```
module add16 ( input[15:0] a, input[15:0] b, input cin, output[15:0] sum, output cout );
```

Within each add16, 16 full adders (module add1, not provided) are instantiated to actually perform the addition. You must write the full adder module that has the following declaration:

```
module add1 ( input a, input b, input cin, output sum, output cout );
```

Recall that a full adder computes the sum and carry-out of $a+b+cin$.

In summary, there are three modules in this design:


top_module — Your top-level module that contains two of...

add16, provided — A 16-bit adder module that is composed of 16 of...

add1 — A 1-bit full adder module.

Ans;
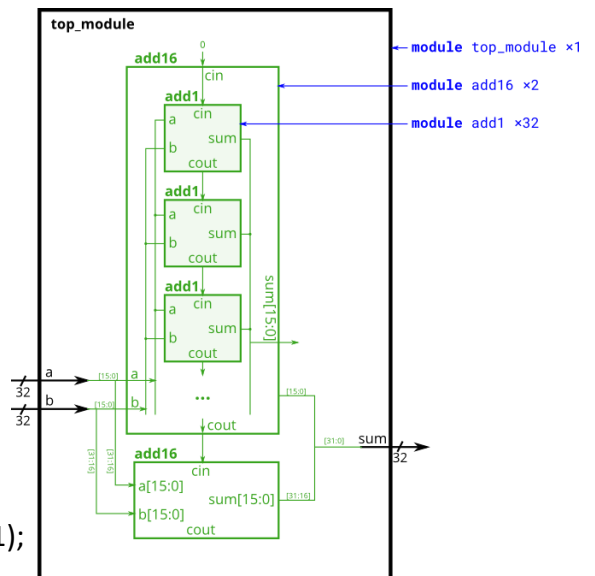
```
module top_module (
    input [31:0] a,
    input [31:0] b,
    output [31:0] sum
);
    wire con1, con2;
    add16 adder_1(a[15:0], b[15:0], 0, sum[15:0], con1);
    add16 adder_2(a[31:16], b[31:16], con1, sum[31:16], con2);
endmodule
```




```
module add1 ( input a, input b, input cin, output sum, output cout );
```

```
    assign sum = a^b^cin;
```

```
    assign cout = (a&b)|(a&cin)|(b&cin);
```

```
endmodule
```

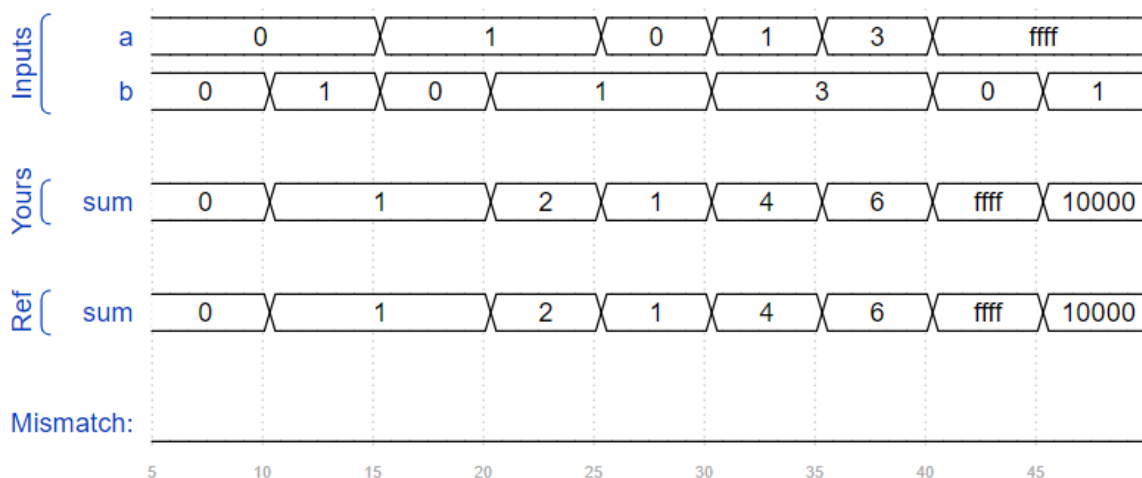

28. In this exercise, you are provided with the same module `add16` as the previous exercise, which adds two 16-bit numbers with carry-in and produces a carry-out and 16-bit sum. You must instantiate three of these to build the carry-select adder, using your own 16-bit 2-to-1 multiplexer.

Connect the modules together as shown in the diagram below. The provided module `add16` has the following declaration:

```
module add16 ( input[15:0] a, input[15:0] b, input cin, output[15:0] sum, output cout );
ans;
```

```
module top_module(
    input [31:0] a,
    input [31:0] b,
    output reg [31:0] sum
);
```

```
    wire [15:0] cout,con2;
```

```
    wire [15:0]alt_sum1, alt_sum2;
```

```
    add16 adder1(a[15:0], b[15:0], 0, sum[15:0], cout);
```

```
    add16 adder_sel1(a[31:16], b[31:16], 0, alt_sum1, con2);
```

```
    add16 adder_sel2(a[31:16], b[31:16], 1, alt_sum2, con2);
```

```
    always @(cout, alt_sum1, alt_sum2) begin
```

```
        case(cout)
```



```
            0 : sum[31:16] = alt_sum1;
```

```
            1 : sum[31:16] = alt_sum2;
```

```
        endcase
```

```
    end
```


```
endmodule
```

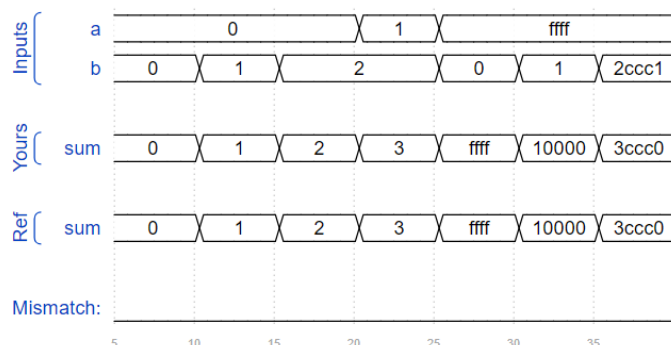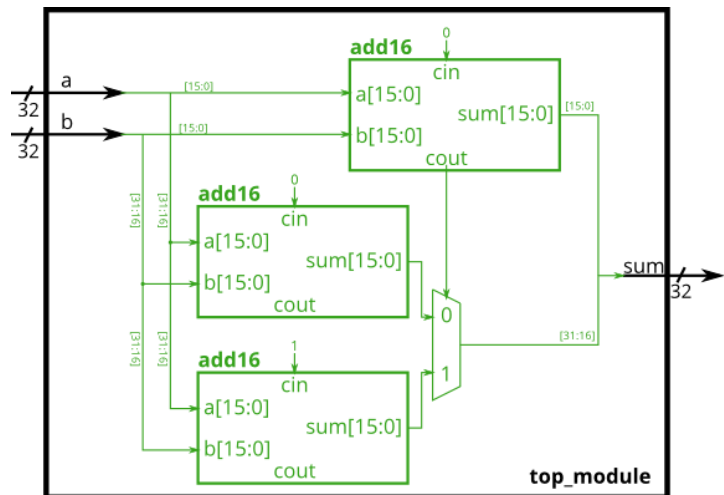

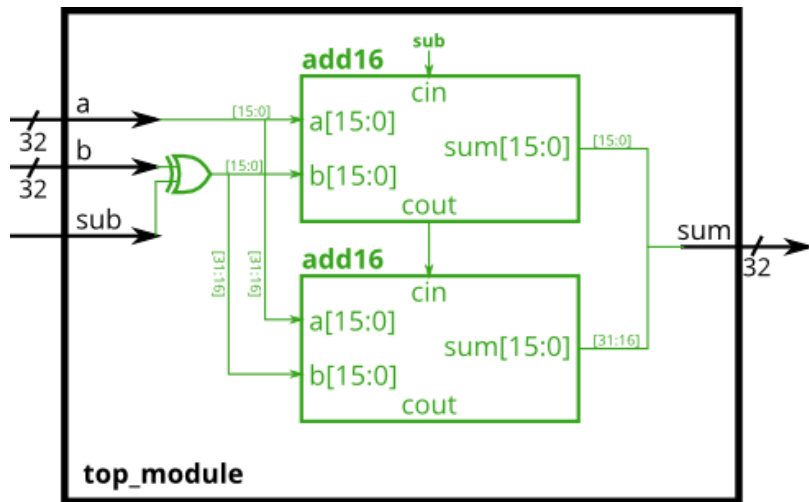29. Build the adder-subtractor below.

You are provided with a 16-bit adder module, which you need to instantiate twice:

```
module add16 ( input[15:0] a, input[15:0] b, input cin, output[15:0] sum, output cout );
```



Ans;

```
module top_module(
```

```
    input [31:0] a,
```

```
    input [31:0] b,
```

```
    input sub,
```

```
    output [31:0] sum
```

```
);
```

```
    wire wire1;
```


```
    wire [31:0] b_xor;
```

```
    assign b_xor = {32{sub}}^b;
```

```
    add16 adder1(a[15:0], b_xor[15:0], sub, sum[15:0], wire1);
```

```
    add16 adder2(a[31:16], b_xor[31:16], wire1, sum[31:16]);
```

```
endmodule
```

 

30. Build an AND gate using both an assign statement and a combinational always block. (Since assign statements and combinational always blocks function identically, there is no way to enforce that you're using both methods. But you're here for practice, right?...)

Ans;


```
module top_module(
```

```
    input a,
```

```
    input b,
```

```
    output wire out_assign,
```


```
    output reg out_alwaysblock
```

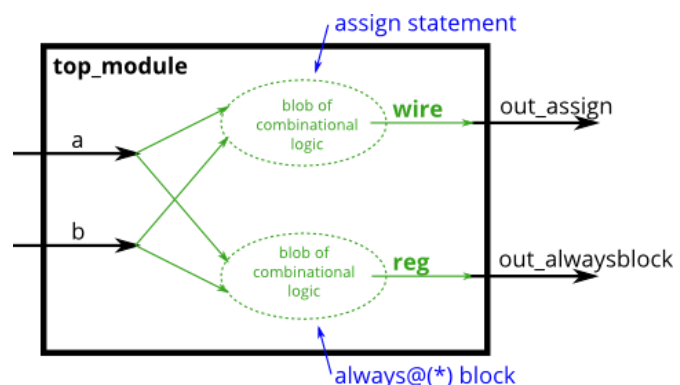


```

);
    assign out_assign = a&&b;
    always @(*) begin
        out_alwaysblock = a&&b;
    end
endmodule

```

 

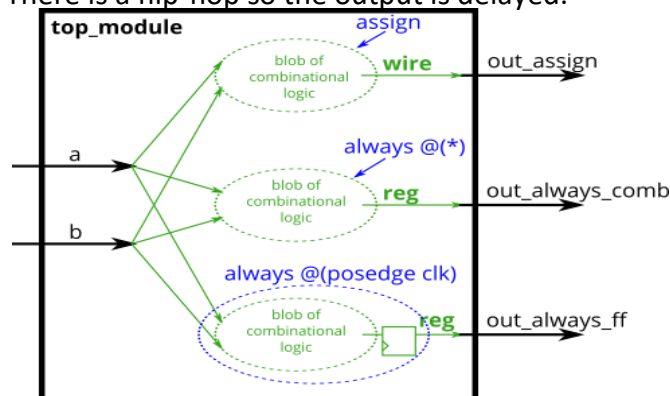31. Build an XOR gate three ways, using an assign statement, a combinational always block, and a clocked always block. Note that the clocked always block produces a different circuit from the other two: There is a flip-flop so the output is delayed.




Ans;

```

module top_module(
    input clk,
    input a,
    input b,
    output wire out_assign,
    output reg out_always_comb,
    output reg out_always_ff );
    assign out_assign = a^b;
    always @ (*) begin
        out_always_comb = a^b;
    end
    always @ (posedge clk) begin
        out_always_ff <= a^b;
    end
endmodule

```

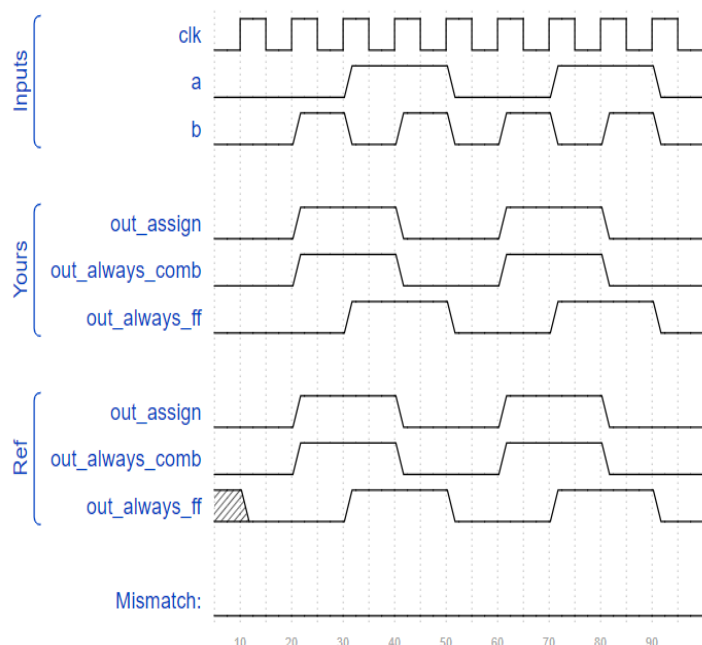

32. Build a 2-to-1 mux that chooses between a and b. Choose b if both sel_b1 and sel_b2 are true. Otherwise, choose a. Do the same twice, once using assign statements and once using a procedural if statement.

Ans;

```
module top_module(
```

```
    input a,
```

```
    input b,
```

```
    input sel_b1,
```

```
    input sel_b2,
```

```
    output wire out_assign,
```

```
    output reg out_always );
```

```
    assign out_assign = (sel_b1 == 1'b1 && sel_b2 == 1'b1) ? b : a;
```

```
    always @(*) begin
```

```
        if (sel_b1 == 1'b1 && sel_b2 == 1'b1) begin
```

```
            out_always = b;
```

```
        end
```

```
        else begin
```


```
            out_always = a;
```

```
        end
```

```
    end
```

```
endmodule
```

sel_b1	sel_b2	out_assign out_always
0	0	a
0	1	a
1	0	a
1	1	b

 

33. The following code contains incorrect behaviour that creates a latch. Fix the bugs so that you will shut off the computer only if it's really overheated, and stop driving if you've arrived at your destination or you need to refuel.

```
always @(*) begin
```


```
    if (cpu_overheated)
```

```
        shut_off_computer = 1;
```

```
end
```

```
always @(*) begin
```

```
    if (~arrived)
```

 

```

    keep_driving = ~gas_tank_empty;
end

```

ans;

```

module top_module (

```

```

    input  cpu_overheated,
    output reg shut_off_computer,

```

```

    input  arrived,

```

```

    input  gas_tank_empty,

```

```

    output reg keep_driving );

```

```

always @(*) begin

```

```

    if (cpu_overheated)

```

```

        shut_off_computer = 1;

```

```

    else

```

```

        shut_off_computer = 0; // Fix: Ensure shut_off_computer is driven to 0 when not
overheated

```

```

end

```

```

always @(*) begin

```

```

    if (~arrived)

```

```

        keep_driving = ~gas_tank_empty;

```

```

    else

```

```

        keep_driving = 0; // Fix: Ensure keep_driving is driven to 0 when arrived

```

```


end

```

```

endmodule

```

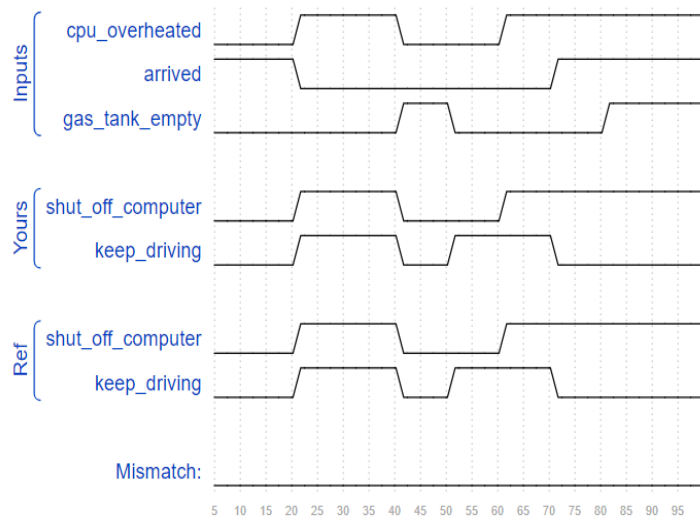

34. Case statements are more convenient than if statements if there are a large number of cases. So, in this exercise, create a 6-to-1 multiplexer. When `sel` is between 0 and 5, choose the corresponding data input. Otherwise, output 0. The data inputs and outputs are all 4 bits wide.

Ans;

```

module top_module (

```

```


    input [2:0] sel,

```

```

input [3:0] data0,
input [3:0] data1,
input [3:0] data2,
input [3:0] data3,
input [3:0] data4,
input [3:0] data5,
output reg [3:0] out );
always@(*) begin
    case(sel)
        3'b000: out = data0;
        3'b001: out = data1;
        3'b010: out = data2;
        3'b011: out = data3;
        3'b100: out = data4;
        3'b101: out = data5;
        default: out = 4'b0000;
    endcase
end
endmodule

```

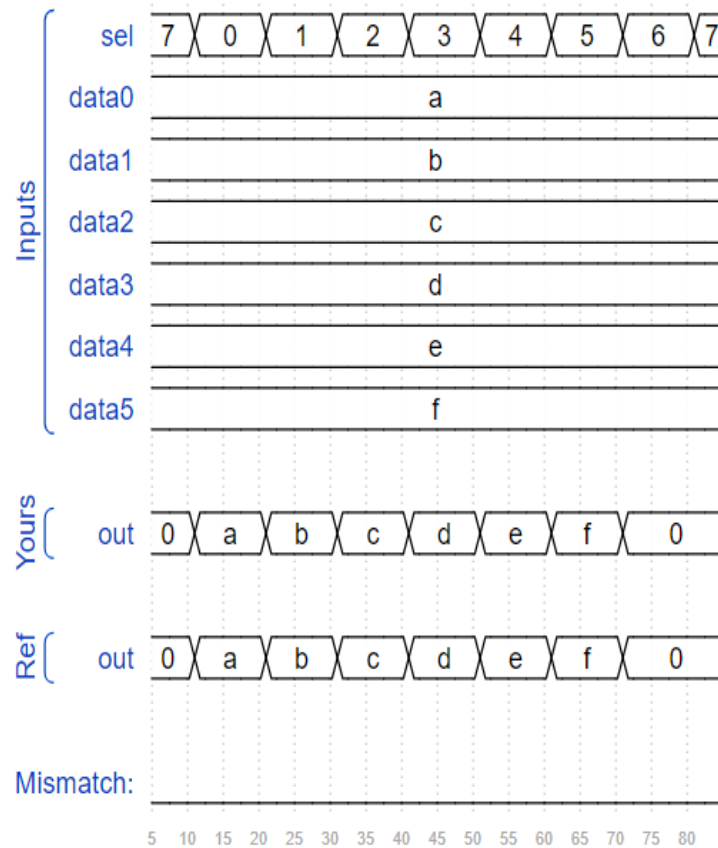

35. Build a 4-bit priority encoder. For this problem, if none of the input bits are high (i.e., input is zero), output zero. Note that a 4-bit number has 16 possible combinations.

Ans;

```

module top_module (
    input [3:0] in,
    output reg [1:0] pos );
always @(*) begin
    if (in[0]==1'b1)
        pos = 0;
    else if (in[1]==1'b1)
        pos = 1;

```

```
else if (in[2]==1'b1)
```

```
    pos = 2;
```

```
else if (in[3]==1'b1)
```


```
    pos = 3;
```

```
else
```

```
    pos = 0;
```

```
end
```

```
endmodule
```

 

36. Build a priority encoder for 8-bit inputs. Given an 8-bit vector, the output should report the first (least significant) bit in the vector that is 1. Report zero if the input vector has no bits that are high. For example, the input 8'b10010000 should output 3'd4, because bit[4] is first bit that is high.

Ans;

```
module top_module (
```

```
    input [7:0] in,
```

```
    output reg [2:0] pos );
```

```
always @(*) begin
```

```
    casez (in[7:0])
```

```
        8'bzzzzzz1: pos = 0;
```

```
        8'bzzzzz1z: pos = 1;
```

```
        8'bzzzzz1zz: pos = 2;
```

```
        8'bzzzz1zzz: pos = 3;
```

```
        8'bzzz1zzzz: pos = 4;
```

```
        8'bzz1zzzzz: pos = 5;
```

```
        8'bz1zzzzzz: pos = 6;
```


```
        8'b1zzzzzzz: pos = 7;
```

```
        default:      pos = 0;
```

```
    endcase
```

```
end
```

```
endmodule
```

 

37. you're building a circuit to process scancodes from a PS/2 keyboard for a game. Given the last two bytes of scancodes received, you need to indicate whether one of the arrow keys on the keyboard have been pressed. This involves a fairly simple mapping, which can be implemented as a case statement (or if-elseif) with four cases.

Scancode [15:0]	Arrow key
16'h06b	left arrow
16'h072	down arrow
16'h074	right arrow
16'h075	up arrow
Anything else	none

Build this circuit that recognizes these four scancodes and asserts the correct output.

Ans;

```


module top_module (
    input [15:0] scancode,
    output reg left,
    output reg down,
    output reg right,
    output reg up );
always @ (scancode) begin
    up = 1'b0; down = 1'b0; left = 1'b0; right = 1'b0;
    case (scancode)
        16'h06b:begin
            up = 1'b0; down = 1'b0; left = 1'b1; right = 1'b0;
        end
        16'h072:begin
            up = 1'b0; down = 1'b1; left = 1'b0; right = 1'b0;
        end
        16'h074:begin
            up = 1'b0; down = 1'b0; left = 1'b0; right = 1'b1;
    
```



```

end
16'he075:begin
    up = 1'b1; down = 1'b0; left = 1'b0; right = 1'b0;
end
endcase
end
endmodule

```

 


38. Given four unsigned numbers, find the minimum. Unsigned numbers can be compared with standard comparison operators ($a < b$). Use the conditional operator to make two-way min circuits, then compose a few of them to create a 4-way min circuit. You'll probably want some wire vectors for the intermediate results.

Ans;

```

module top_module (
    input [7:0] a, b, c, d,
    output [7:0] min);
    wire [7:0] int1, int2;
    assign int1 = (a < b)? a:b;
    assign int2 = (int1 < c)? int1:c;
    assign min = (int2 < d)? int2:d;
endmodule

```

 

39. Parity checking is often used as a simple method of detecting errors when transmitting data through an imperfect channel. Create a circuit that will compute a parity bit for a 8-bit byte (which will add a 9th bit to the byte). We will use "even" parity, where the parity bit is just the XOR of all 8 data bits.

Expected solution length: Around 1 line.

Ans;

```
module top_module (
    input [7:0] in,
    output parity);
    assign parity = ^in;
endmodule
```

40. Build a combinational circuit with 100 inputs, in[99:0].

There are 3 outputs:

out_and: output of a 100-input AND gate.

out_or: output of a 100-input OR gate.

out_xor: output of a 100-input XOR gate.

Ans;


```
module top_module(
    input [99:0] in,
    output out_and,
    output out_or,
    output out_xor
);
```

```
    assign out_and = &in;
```

```
    assign out_or = |in;
```

```
    assign out_xor = ^in;
```

```
endmodule
```

 

41. Given a 100-bit input vector [99:0], reverse its bit ordering.

Ans;

```
module top_module(
```

```

input [99:0] in,
output [99:0] out
);
integer i;
always @ (in) begin
    for (i=0;i<100; i=i+1) begin
        out[99-i] = in[i];
    end
end
endmodule

```


42. A "population count" circuit counts the number of '1's in an input vector. Build a population count circuit for a 255-bit input vector.

Ans;

```

module top_module(
    input [254:0] in,
    output [7:0] out );
    integer i;
    reg [7:0] counter;
    always @ (in) begin
        counter = 0;    for (i=0; i<255; i=i+1) begin
            if (in[i]==1'b1)
                counter = counter+1'b1;
        end
        out = counter;
    end
endmodule

```

 

43. Create a 100-bit binary ripple-carry adder by instantiating 100 full adders. The adder adds two 100-bit numbers and a carry-in to produce a 100-bit sum and carry out. To encourage you to actually instantiate full adders, also output the carry-out from each full adder in the ripple-carry adder. cout[99] is the final carry-out from the last full adder, and is the carry-out you usually see

Ans;

```
module one_bit_FA(
    input a,b,
    input cin,
    output cout,sum);

    assign sum = a^b^cin;
    assign cout = (a&b)|(b&cin)|(cin&a);
endmodule

module top_module(
    input [99:0] a, b,
    input cin,
    output [99:0] cout,
    output [99:0] sum );
    genvar i;
    one_bit_FA FA1(a[0],b[0],cin,cout[0],sum[0]);
    for (i=1; i<100; i=i+1) begin : Full_adder_block
        one_bit_FA FA(a[i],b[i],cout[i-1],cout[i],sum[i]);
    end
endgenerate
endmodule
```

44. You are provided with a BCD one-digit adder named bcd_fadd that adds two BCD digits and carry-in, and produces a sum and carry-out.

```
module bcd_fadd (
    input [3:0] a,
    input [3:0] b,
    input cin,
    output cout,
    output [3:0] sum );
```

Instantiate 100 copies of bcd_fadd to create a 100-digit BCD ripple-carry adder. Your adder should add two 100-digit BCD numbers (packed into 400-bit vectors) and a carry-in to produce a 100-digit sum and carry out.

Ans;

```
module top_module(
    input [399:0] a, b,
    input cin,
    output cout,
    output [399:0] sum );
    wire[99:0] cout_wires;
    genvar i;
    generate
        bcd_fadd(a[3:0], b[3:0], cin, cout_wires[0],sum[3:0]);
        for (i=4; i<400; i=i+4) begin: bcd_adder_instances
            bcd_fadd bcd_adder(a[i+3:i], b[i+3:i], cout_wires[i/4-1],cout_wires[i/4],sum[i+3:i]);
        end
    endgenerate
    assign cout = cout_wires[99];
endmodule
```


45. Implement the following circuit:

in ————— out

Ans;

```
module top_module (
    input in,
    output out);
    assign out = in;
endmodule
```


46. Implement the following circuit:

 

Ans;

```
module top_module (  
    output out);  
    assign out = 1'b0;  
endmodule
```

47. Implement the following circuit:

 

Ans;

```
module top_module (  
    input in1,  
    input in2,  
    output out);  
    assign out = ~(in1 | in2);  
endmodule
```


48. Implement the following circuit:



Ans;

```
module top_module (  
    input in1,  
    input in2,  
    output out);  
    assign out = in1 & ~in2;  
endmodule
```

49. Implement the following circuit:

 

Ans;

```
module top_module (  
    input in1,  
    input in2,  
    input in3,  
    output out);  
    wire wire1;  
    assign wire1 = ~(in1 ^ in2);  
    assign out = wire1 ^ in3;  
endmodule
```

50. Build a combinational circuit with two inputs, a and b.

There are 7 outputs, each with a logic gate driving it:

out_and: a and b

out_or: a or b

out_xor: a xor b

out_nand: a nand b

```

out_nor: a nor b
out_xnor: a xnor b
out_anotb: a and-not b
ans;

```

```

module top_module(

```

```

    input a, b,
    output out_and,
    output out_or,
    output out_nand,
    output out_nor,
    output out_xnor,
    output out_anotb

```

```

);

```

```


    assign out_and = a && b;
    assign out_or = a || b;
    assign out_xor = a ^ b;
    assign out_nand = ~(a&&b);
    assign out_nor = ~(a || b);
    assign out_xnor = ~(a^b);
    assign out_anotb = a&&~b;

```

```


endmodule

```

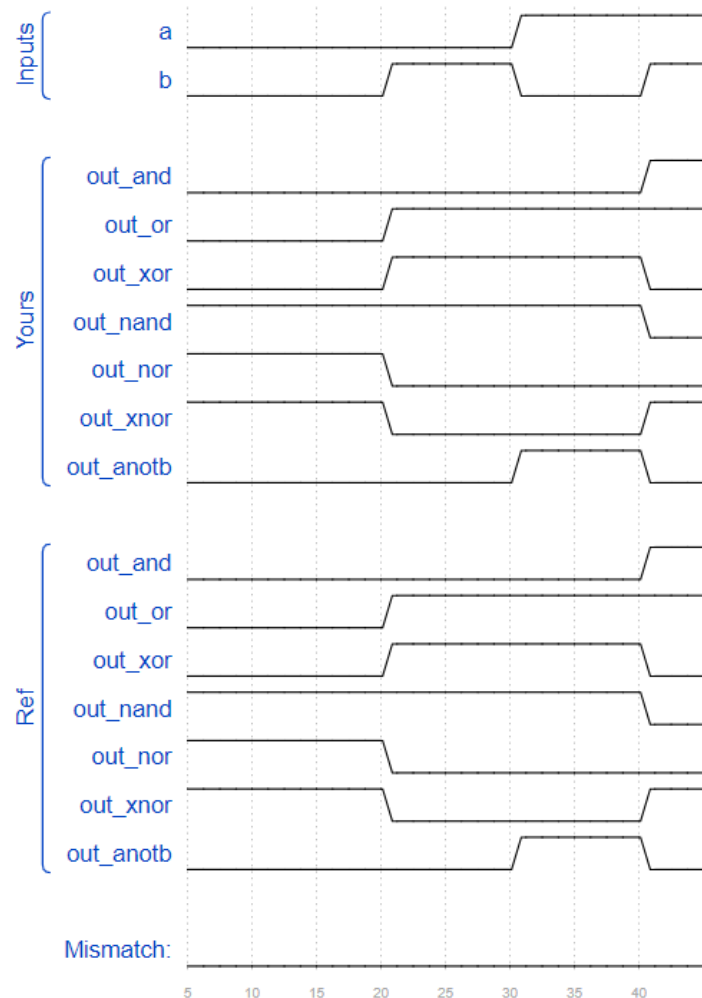

 51. The 7400-series integrated circuits are a series of digital chips with a few gates each. The 7420 is a chip with two 4-input NAND gates.

Create a module with the same functionality as the 7420 chip. It has 8 inputs and 2 outputs.




Ans;

```
module top_module (
    input p1a, p1b, p1c, p1d,
    output p1y,
    input p2a, p2b, p2c, p2d,
    output p2y );
```


```
    assign p1y = ~(p1a && p1b && p1c && p1d);
```

```
    assign p2y = ~(p2a && p2b && p2c && p2d);
```

```
endmodule
```

 

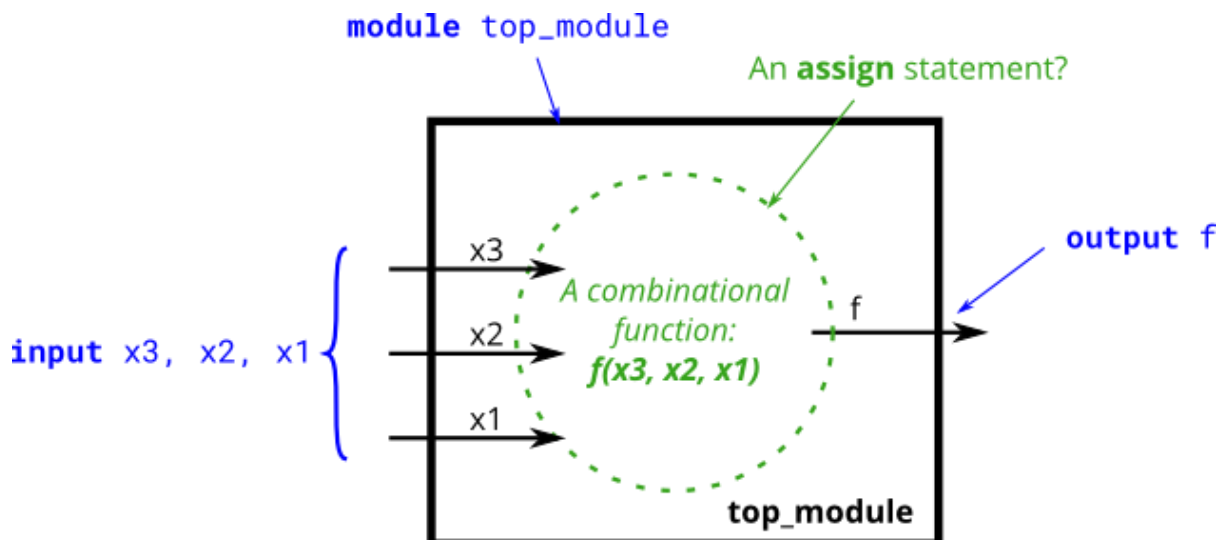52. Create a combinational circuit that implements the above truth table.



Ans;

```
module top_module(
```

```
    input x3,
```

```
    input x2,
```


```
    input x1,
```

```
    output f
```

```
);
```

```
    assign f = (~x3&x2&~x1) | (~x3&x2&x1) | (x3&~x2&x1) | (x3&x2&x1);
```

```
endmodule
```

 

53. Create a circuit that has two 2-bit inputs A[1:0] and B[1:0], and produces an output z. The value of z should be 1 if A = B, otherwise z should be 0.

Ans;

```
module top_module ( input [1:0] A, input [1:0] B, output z );
```

```
    assign z = (A==B);
```

```
endmodule
```

54. Module A is supposed to implement the function $z = (x^y) \& x$. Implement this module.


Ans;

```
module top_module (input x, input y, output z);
```

```
    assign z = (x^y) & x;
```

```
endmodule
```

 55. Circuit B can be described by the following simulation waveform: Mt2015 q4b.png




Ans;


```
module top_module ( input x, input y, output z );
```

```
    assign z = ~(x^y);
```

```
endmodule
```

 

 56. The top-level design consists of two instantiations each of subcircuits A and B, as shown below.



Implement this circuit.

Ans;

```
module top_module (input x, input y, output z);
```

```
    wire z1, z2, z3, z4,z5,z6;
```

```
    A IA1(x,y,z1);
```

```
    B IB1(x,y,z2);
```

```
    A IA2(x,y,z3);
```

```
    B IB2(x,y,z4);
```

```
    assign z5 = z1 | z2;
```

```
    assign z6 = z3 & z4;
```

```
    assign z = z5 ^ z6;
```

```
endmodule
```

```
module B( input x, input y, output z );
```

```
    assign z= ~(x^y);
```

```
endmodule
```

```
module A(input x, input y, output z);
```

```
    assign z = (x^y) & x;
```

```
endmodule
```


57. Suppose you are designing a circuit to control a cellphone's ringer and vibration motor.

Whenever the phone needs to ring from an incoming call (input ring), your circuit must either turn on the ringer (output ringer = 1) or the motor (output motor = 1), but not both. If the phone is in vibrate mode (input vibrate_mode = 1), turn on the motor. Otherwise, turn on the ringer.

Try to use only assign statements, to see whether you can translate a problem description into a collection of logic gates.


Design hint: When designing circuits, one often has to think of the problem "backwards", starting from the outputs then working backwards towards the inputs. This is often the opposite of how one would think about a (sequential, imperative) programming problem, where one would look at the inputs first then decide on an action (or output). For sequential programs, one would often think "If (inputs are ___) then (output should be ___)". On the other hand, hardware designers often think "The (output should be ___) when (inputs are ___)".

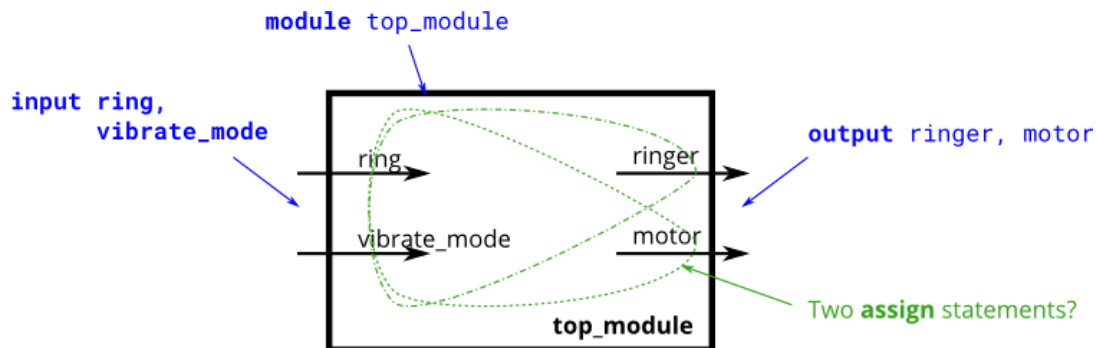The above problem description is written in an imperative form suitable for software programming (if ring then do this), so you must convert it to a more declarative form suitable for hardware implementation (assign ringer = ___). Being able to think in, and translate between, both styles is one of the most important skills needed for hardware design.



Ans;
 
```
module top_module (
    input ring,
    input vibrate_mode,
    output ringer,    // sound
    output motor      // Vibrate
);
    assign motor = vibrate_mode && ri
    assign ringer = (~vibrate_mode) && ring;
endmodule
```



58. A heating/cooling thermostat controls both a heater (during winter) and an air conditioner (during summer). Implement a circuit that will turn on and off the heater, air conditioning, and blower fan as appropriate.

The thermostat can be in one of two modes: heating (mode = 1) and cooling (mode = 0). In heating mode, turn the heater on when it is too cold (too_cold = 1) but do not use the air conditioner. In cooling mode, turn the air conditioner on when it is too hot (too_hot = 1), but do not turn on the heater. When the heater or air conditioner are on, also turn on the fan to circulate the air. In

addition, the user can also request the fan to turn on (fan_on = 1), even if the heater and air conditioner are off.

Try to use only assign statements, to see whether you can translate a problem description into a collection of logic gates.

Ans;


```
module top_module (
    input too_cold,
    input too_hot,
    input mode,
    input fan_on,
    output heater,
    output aircon,
    output fan
);
```

```
    assign heater = mode && too_cold;
```


```
    assign aircon = (~mode) && too_hot;
```

```
    assign fan = aircon || heater || fan_on;
```

```
endmodule
```

 

Summer

 

59. A "population count" circuit counts the number of '1's in an input vector. Build a population count circuit for a 3-bit input vector.


Ans;

```
module top_module(
    input [2:0] in,
    output [1:0] out );
    integer i,count;
    always @ * begin
        count = 0;
```

```

for (i=0; i<3;i=i+1) begin
    if (in[i]==1'b1) count=count+1;
end
out = count;
end
endmodule

```

 

60. You are given a four-bit input vector in[3:0]. We want to know some relationships between each bit and its neighbour:

out_both: Each bit of this output vector should indicate whether both the corresponding input bit and its neighbour to the left (higher index) are '1'. For example, out_both[2] should indicate if in[2] and in[3] are both 1. Since in[3] has no neighbour to the left, the answer is obvious so we don't need to know out_both[3].

out_any: Each bit of this output vector should indicate whether any of the corresponding input bit and its neighbour to the right are '1'. For example, out_any[2] should indicate if either in[2] or in[1] are 1. Since in[0] has no neighbour to the right, the answer is obvious so we don't need to know out_any[0].


out_different: Each bit of this output vector should indicate whether the corresponding input bit is different from its neighbour to the left. For example, out_different[2] should indicate if in[2] is different from in[3]. For this part, treat the vector as wrapping around, so in[3]'s neighbour to the left is in[0].

Ans;

```

module top_module(
    input [3:0] in,
    output [2:0] out_both,
    output [3:1] out_any,
    output [3:0] out_different );
    assign out_both    = in[2:0] & in[3:1];
    assign out_any     = in[3:1] | in[2:0];
    assign out_different = in ^ {in[0],in[3:1]};
endmodule

```

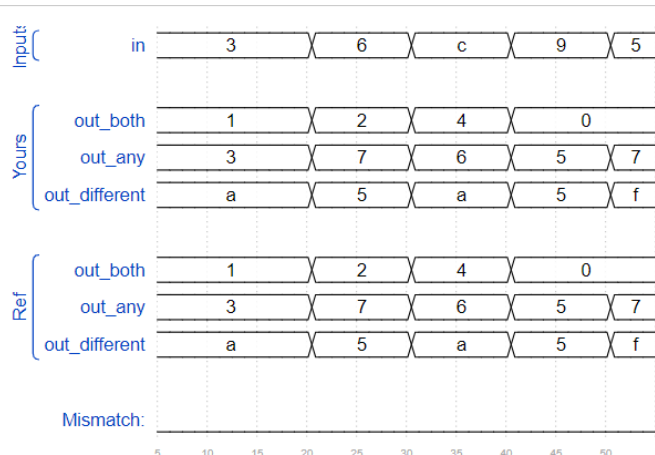

61. You are given a 100-bit input vector in[99:0]. We want to know some relationships between each bit and its neighbour:

out_both: Each bit of this output vector should indicate whether both the corresponding input bit and its neighbour to the left are '1'. For example, out_both[98] should indicate if in[98] and in[99] are both 1. Since in[99] has no neighbour to the left, the answer is obvious so we don't need to know out_both[99].

out_any: Each bit of this output vector should indicate whether any of the corresponding input bit and its neighbour to the right are '1'. For example, out_any[2] should indicate if either in[2] or in[1] are 1. Since in[0] has no neighbour to the right, the answer is obvious so we don't need to know out_any[0].

out_different: Each bit of this output vector should indicate whether the corresponding input bit is different from its neighbour to the left. For example, out_different[98] should indicate if in[98] is different from in[99]. For this part, treat the vector as wrapping around, so in[99]'s neighbour to the left is in[0].


Ans;

```
module top_module(
    input [99:0] in,
    output [98:0] out_both,
    output [99:1] out_any,
    output [99:0] out_different );
    assign out_both    = in[98:0] & in[99:1];
    assign out_any     = in[99:1] | in[98:0];
    assign out_different = in ^ {in[0],in[99:1]};
endmodule
```

 62. Create a one-bit wide, 2-to-1 multiplexer. When sel=0, choose a. When sel=1, choose b.


Ans;

```
module top_module(
    input a, b, sel,
    output out );
    assign out = sel?b:a;
endmodule
```




63. Create a 100-bit wide, 2-to-1 multiplexer. When sel=0, choose a. When sel=1, choose b.

Ans;

 

64. Create a 16-bit wide, 9-to-1 multiplexer. sel=0 chooses a, sel=1 chooses b, etc. For the unused cases (sel=9 to 15), set all output bits to '1'.

Ans;

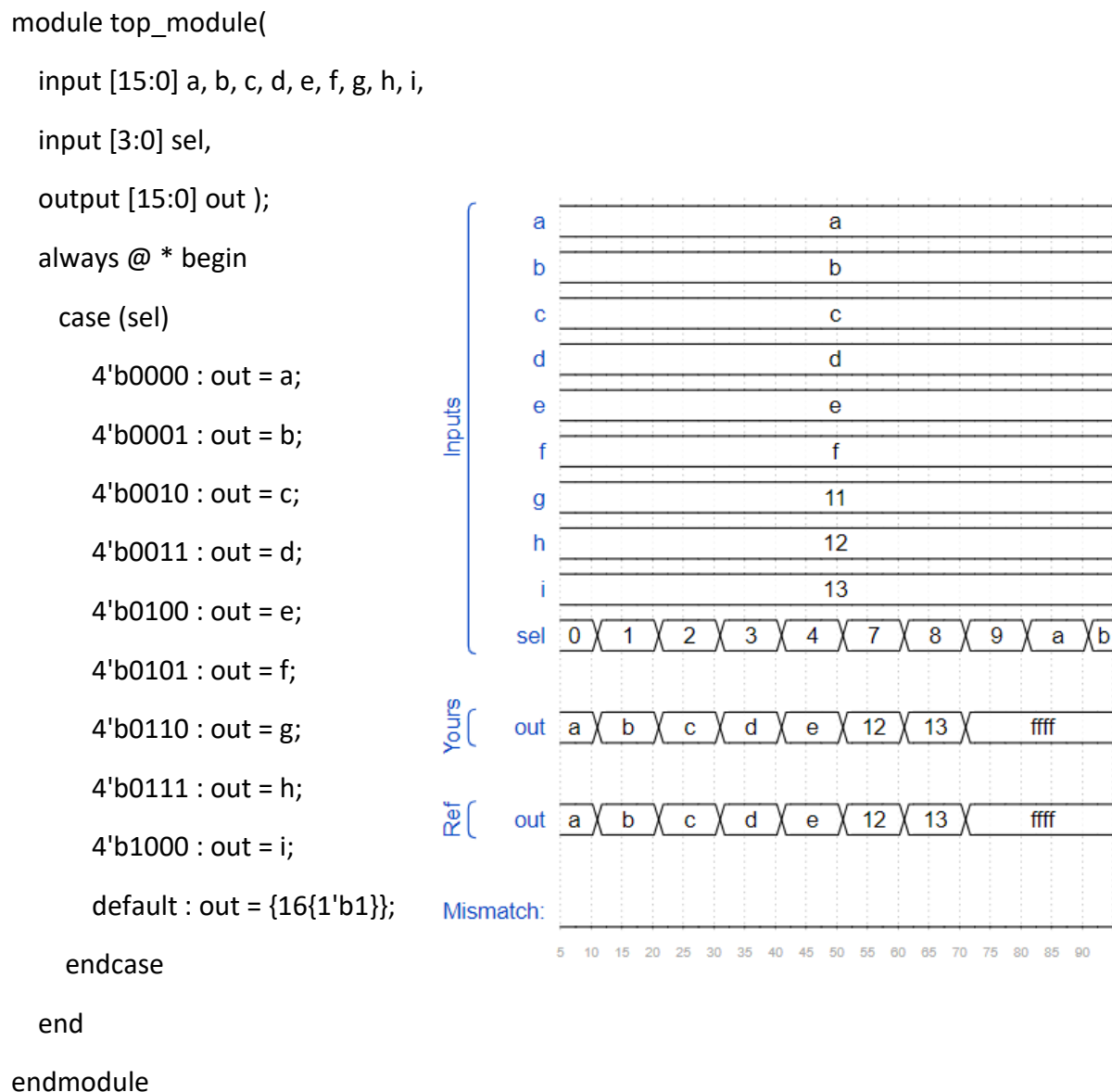

65. Create a 1-bit wide, 256-to-1 multiplexer. The 256 inputs are all packed into a single 256-bit input vector. sel=0 should select in[0], sel=1 selects bits in[1], sel=2 selects bits in[2], etc.

Ans;

```
module top_module(  
    input [255:0] in,  
    input [7:0] sel,  
    output out  
);  
assign out = in[sel];  
endmodule
```

66. Create a 4-bit wide, 256-to-1 multiplexer. The 256 4-bit inputs are all packed into a single 1024-bit input vector. sel=0 should select bits in[3:0], sel=1 selects bits in[7:4], sel=2 selects bits in[11:8], etc.

Ans;

```
module top_module(  
    input [1023:0] in,  
    input [7:0] sel,  
    output [3:0] out );  
integer range;  
wire [7:0] con1;  
always @ (*) begin  
    range = sel;  
    out = in[sel*4 +:4];  
end  
endmodule
```

67. Create a half adder. A half adder adds two bits (with no carry-in) and produces a sum and carry-out.

Ans;

```
module top_module(  
    input a, b,  
    output cout, sum );
```

```
assign sum = a^b;
```

```
assign cout = a&b;
```

```
endmodule
```

68. Create a full adder. A full adder adds three bits (including carry-in) and produces a sum and carry-out.

Ans;

```
module top_module(
```


```
    input a, b, cin,
```

```
    output cout, sum );
```

```
    assign cout = a&b | b&cin | a&cin;
```

```
    assign sum = a^b^cin;
```

```
endmodule
```

 

69. ripple carry adder 3-bit.

Ans;

```
module top_module(
```

```
    input [2:0] a, b,
```

```
    input cin,
```


```
    output [2:0] cout,
```

```
    output [2:0] sum );
```


```

FA FA1(a[0],b[0],cin,cout[0],sum[0]);
FA FA2(a[1],b[1],cout[0],cout[1],sum[1]);
FA FA3(a[2],b[2],cout[1],cout[2],sum[2]);
endmodule
module FA(
    input a, b, cin,
    output cout, sum );
    assign cout = a&b | b&cin | a&cin;
    assign sum = a^b^cin;
endmodule

```

 

70. Implement the following circuit:

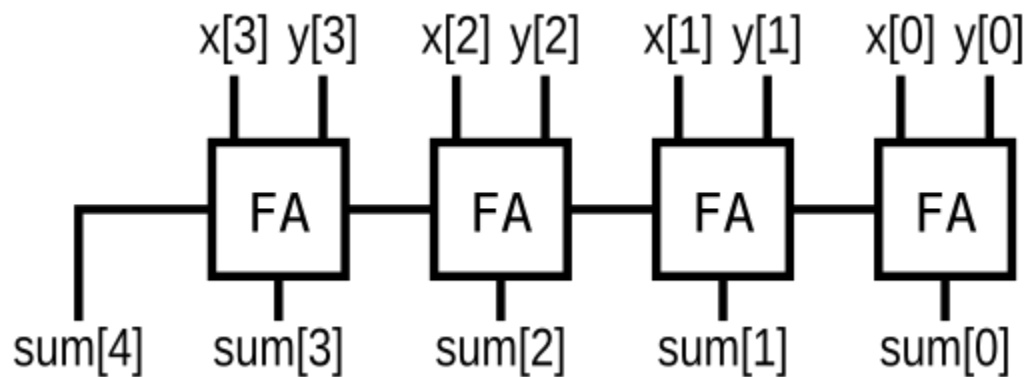

Ans;

```

module top_module (
    input [3:0] x,
    input [3:0] y,
    output [4:0] sum);
    wire [3:0] cout;
    FA FA1(x[0],y[0],0,cout[0],sum[0]);
    FA FA2(x[1],y[1],cout[0],cout[1],sum[1]);
    FA FA3(x[2],y[2],cout[1],cout[2],sum[2]);
    FA FA4(x[3],y[3],cout[2],sum[4],sum[3]);
endmodule

```

```

endmodule

module FA(
    input a, b, cin,
    output cout, sum );

    assign cout = a&b | b&cin | a&cin;

    assign sum = a^b^cin;

endmodule

```

71. Assume that you have two 8-bit 2's complement numbers, a[7:0] and b[7:0]. These numbers are added to produce s[7:0]. Also compute whether a (signed) overflow has occurred.

Ans;

```

module top_module (
    input [7:0] a,
    input [7:0] b,
    output [7:0] s,
    output overflow
);

```

```

    assign s = a+b;

```

```

    assign overflow = a[7]&&b[7]&&(~s[7]) || (~a[7])&&(~b[7])&&(s[7]);

```

```

endmodule

```

```

module top_m(

```

```

    input a, b, cin,

```

```

    output cout, sum );

```

```

    assign cout = a&b | b&cin | a&cin;

```

```

    assign sum = a^b^cin;


```

```

endmodule

```

 72. Create a 100-bit binary adder. The adder adds two 100-bit numbers and a carry-in to produce a 100-bit sum and carry out.



Ans;

```
module top_module(  
    input [99:0] a, b,  
    input cin,  
    output cout,  
    output [99:0] sum );  
  
    genvar i;  
    wire [98:0] con_vect;  
  
    one_bit_FA FA1(a[0],b[0],cin,con_vect[0],sum[0]);  
    one_bit_FA FA2(a[99],b[99],con_vect[98],cout,sum[99]);  
  
    generate  
        for (i=1; i<99; i=i+1) begin : Full_adder_block  
            one_bit_FA FA(a[i],b[i],con_vect[i-1],con_vect[i],sum[i]);  
        end  
    endgenerate  
endmodule  
  
module one_bit_FA(  
    input a,b,  
    input cin,  
    output cout,sum);  
  
    assign sum = a^b^cin;  
    assign cout = (a&b)|(b&cin)|(cin&a);  
endmodule
```

73. You are provided with a BCD (binary-coded decimal) one-digit adder named bcd_fadd that adds two BCD digits and carry-in, and produces a sum and carry-out.

```
module bcd_fadd (  
    input [3:0] a,  
    input [3:0] b,  
    input cin,
```

```
output cout,  
output [3:0] sum );
```

Instantiate 4 copies of `bcd_fadd` to create a 4-digit BCD ripple-carry adder. Your adder should add two 4-digit BCD numbers (packed into 16-bit vectors) and a carry-in to produce a 4-digit sum and carry out.

Ans;


```

module top_module(
    input [15:0] a, b,
    input cin,
    output cout,
    output [15:0] sum );
    wire [2:0] con1;

    bcd_fadd B_add1(a[3:0],b[3:0],cin,con1[0],sum[3:0]);
    bcd_fadd B_add2(a[7:4],b[7:4],con1[0],con1[1],sum[7:4]);
    bcd_fadd B_add3(a[11:8],b[11:8],con1[1],con1[2],sum[11:8]);
    bcd_fadd B_add4(a[15:12],b[15:12],con1[2],cout,sum[15:12]);
endmodule


```

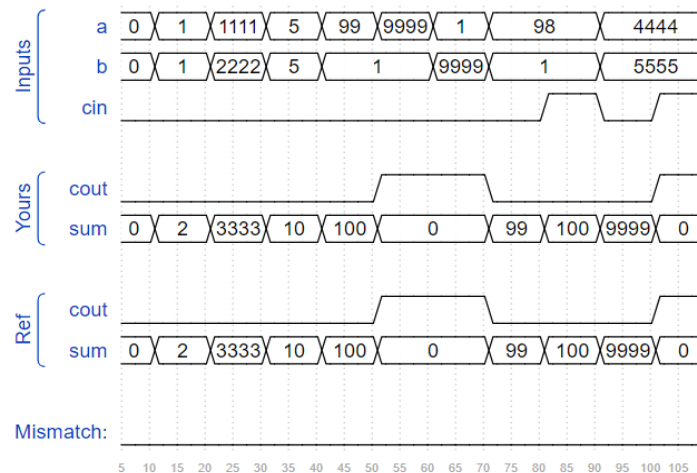The timing diagram illustrates the operation of the BCD adder. The cin signal is a single pulse at time 50. The sum signal is a sequence of BCD digits: 0, 2, 3, 3, 3, 1, 0, 1, 0, 0. The cout signal is a single pulse at time 50. A mismatch is indicated between the sum and cout signals at time 50.



74. Implement the circuit described by the Karnaugh map below.

a \ bc	00	01	11	10
0	0	1	1	1
1	1	1	1	1

 

Ans;

```
module top_module(
    input a,
    input b,
```

```

        input c,
        output out

    );
    assign out = (a | b | c);
endmodule

```

75. Implement the circuit described by the Karnaugh map below.

cd \ ab				
	00	01	11	10
00	1	1	0	1
01	1	0	0	1
11	0	1	1	1
10	1	1	0	0

Ans;

```

module top_module(
    input a,
    input b,
    input c,
    input d,
    output out );

```

```

    assign out = (c | !d | !b) & (!a | !b | c) & (a | b | !c | !d) & (!a | !c | d);


```

```

endmodule

```

 76. Implement the circuit described by the Karnaugh map below.



ab \ cd	01	00	10	11
00	d	0	1	1
01	0	0	d	d
11	0	1	1	1
10	0	1	1	1

Ans;

```
module top_module(
```

```
    input a,
```

```
    input b,
```


```
    input c,
```

```
    input d,
```

```
    output out );
```

```
    assign out = a | (~a & ~b & c);
```

```
endmodule
```

 

77. Implement the circuit described by the Karnaugh map below.

ab \ cd	00	01	11	10
00	0	1	0	1
01	1	0	1	0
11	0	1	0	1
10	1	0	1	0

Ans; module top_module(

input a,

input b,


input c,

input d,

output out);

assign out = a^b^c^d;

endmodule

 

78. A single-output digital system with four inputs (a,b,c,d) generates a logic-1 when 2, 7, or 15 appears on the inputs, and a logic-0 when 0, 1, 4, 5, 6, 9, 10, 13, or 14 appears. The input conditions for the numbers 3, 8, 11, and 12 never occur in this system. For example, 7 corresponds to a,b,c,d being set to 0,1,1,1, respectively.

Determine the output out_sop in minimum SOP form, and the output out_pos in minimum POS form.

Ans;

module top_module (

input a,

input b,

input c,

input d,

output out_sop,

output out_pos

);

assign out_sop = (c&d)|(~a&~b&c);

assign out_pos = c&(~b|~c|d)&(~a|~c|d);

endmodule

79. Consider the function f shown in the Karnaugh map below.

$x_3x_4 \backslash x_1x_2$					
		00	01	11	10
00		d	0	d	d
01		0	d	1	0
11		1	1	d	d
10		1	1	0	d

Ans;

```
module top_module (
    input [4:1] x,
    output f );

    assign f = (x[2]&x[4])|(x[3]&x[4])|(x[3]&~x[1]);

endmodule
```

80. Consider the function f shown in the Karnaugh map below. Implement this function.

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	1	1	1	0
10	1	1	0	1

Ans;


```
module top_module (
    input [4:1] x,
    output f
);

    assign f = (~x[1]&x[3])|(~x[2]&~x[4])|(x[2]&x[3]&x[4]);

endmodule
```

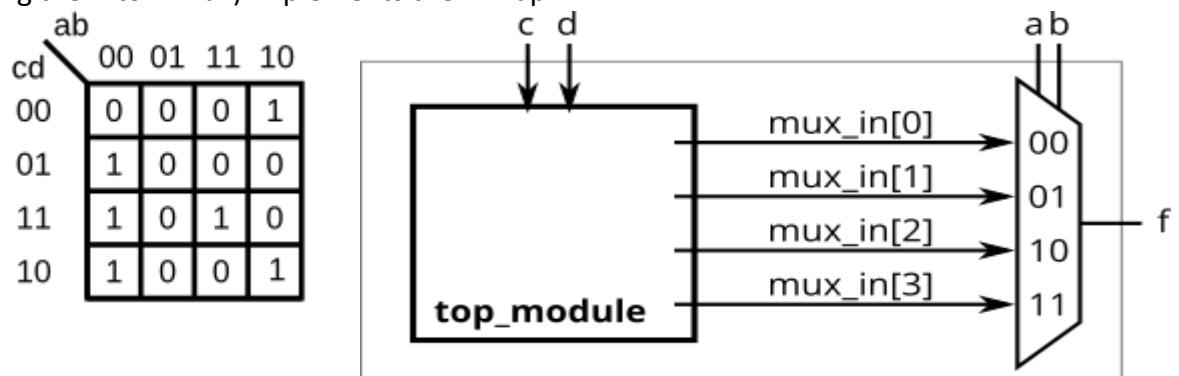81. For the following Karnaugh map, give the circuit implementation using one 4-to-1 multiplexer and as many 2-to-1 multiplexers as required, but using as few as possible. You are not allowed to use any other logic gate and you must use a and b as the multiplexer selector inputs, as shown on the 4-to-1 multiplexer below.

You are implementing just the portion labelled `top_module`, such that the entire circuit (including the 4-to-1 mux) implements the K-map.



Ans;


```

module top_module (
    input c,
    input d,
    output [3:0] mux_in
);


    assign mux_in[0] = c | d;
    assign mux_in[1] = 0;
    assign mux_in[2] = ~d;
    assign mux_in[3] = c & d;

endmodule

```

 

82. Create a single D flip-flop.

 

Ans;


```

module top_module (
    input clk,
    input d,
    output reg q );

    always @ (posedge clk) begin
        q <= d;
    end

endmodule

```

 


83. Create 8 D flip-flops. All DFFs should be triggered by the positive edge of clk.

Ans;

```

module top_module (
    input clk,
    input [7:0] d,

```

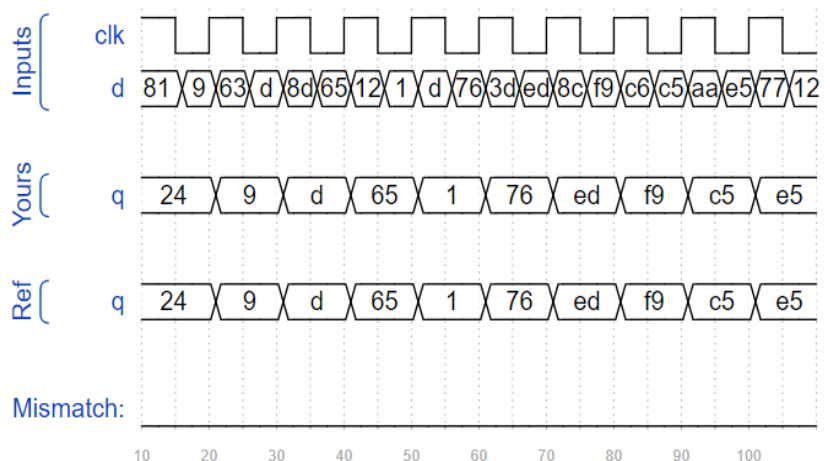

```

    output [7:0] q
);
    always @ (posedge clk) begin
        q <= d;
    end
endmodule

```

84. Create 8 D flip-flops with active high synchronous reset. All DFFs should be triggered by the positive edge of clk.

Ans;

```

module top_module (

```

```

    input clk,
    input reset,
    input [7:0] d,
    output [7:0] q

```

```

);

```

```

always @ (posedge clk) begin

```

```

    if (reset) q<=8'b0;

```

```

    else q <= d;

```

```


end

```

```

endmodule

```

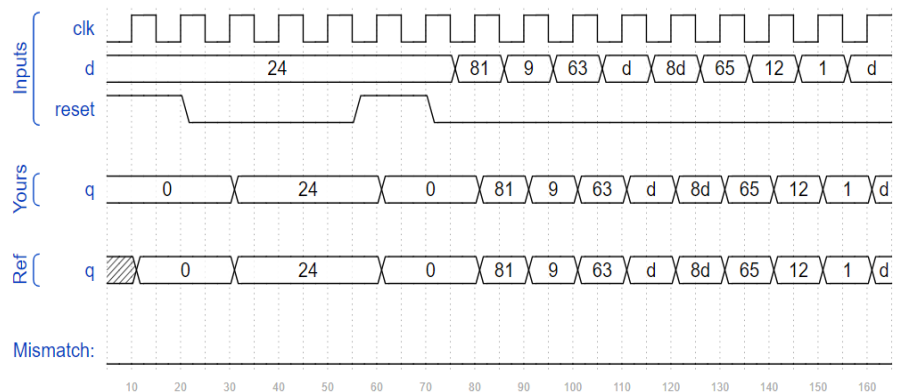

85. Create 8 D flip-flops with active high synchronous reset. The flip-flops must be reset to 0x34 rather than zero. All DFFs should be triggered by the negative edge of clk.

Ans;

```

module top_module (

```

```

    input clk,
    input reset,    input [7:0] d,
    output [7:0] q

```

```

);

```

```


always @ (negedge clk) begin

```

```

    if (reset==1'b1) q<=8'h34;

```

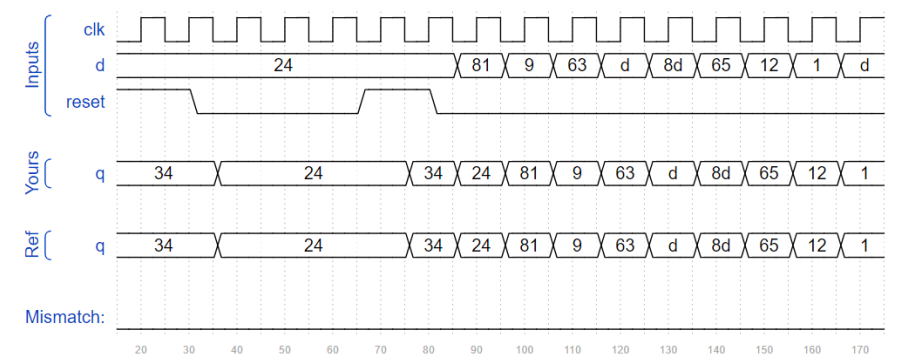

```

        else q <= d;
    end
endmodule

```

86. Create 8 D flip-flops with active high asynchronous reset. All DFFs should be triggered by the positive edge of clk.

Ans;

```

module top_module (

```

```

    input clk,
    input areset,
    input [7:0] d,
    output [7:0] q);

```

```

    always @ (posedge clk or posedge areset ) begin

```

```

        if (areset==1'b1) q<= 1'b0;

```

```

        else q <= d;

```

```


    end

```

```

endmodule

```

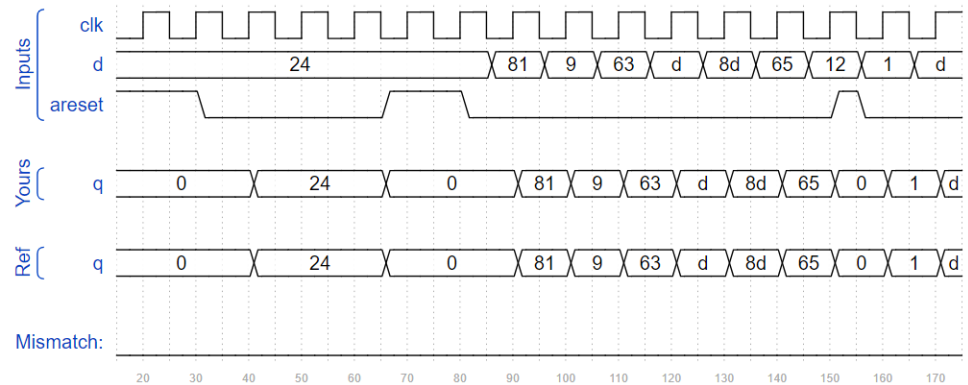

87. Create 16 D flip-flops. It's sometimes useful to only modify parts of a group of flip-flops. The byte-enable inputs control whether each byte of the 16 registers should be written to on that cycle. byteena[1] controls the upper byte d[15:8], while byteena[0] controls the lower byte d[7:0].

resetn is a synchronous, active-low reset.

All DFFs should be triggered by the positive edge of clk.

Ans;

```

module top_module (

```

```

    input clk,
    input resetn,
    input [1:0] byteena,
    input [15:0] d,
    output [15:0] q

```

```


);

```

```

always @ (posedge clk) begin

```

 


```

if (resetn==1'b0) q<= 1'b0;
else begin
    case(byteena)
        2'b00: q    <= q;
        2'b01: q[7:0] <= d[7:0];
        2'b10: q[15:8] <= d[15:8];
        2'b11: q    <= d;
    endcase
end
end endmodule

```

88. Implement the following circuit:

 


Ans;

```

module top_module (
    input d,
    input ena,
    output q);
    always @ (*) begin
        if (ena) q<=d;
    end
endmodule

```

89. Implement the following circuit:

 

Ans;

```

module top_module (


```

```

input clk,
input d,
input ar,
output q);
always @ (posedge clk, posedge ar) begin
    if (ar) q<=1'b0;
    else q<=d;
end
endmodule

```

90. Implement the following circuit:

 


Ans;

```

module top_module (
    input clk,
    input d,
    input r,
    output q);
    always @ (posedge clk) begin
        if (r) q <= 1'b0;
        else q <= d;
    end
endmodule

```


91. Implement the following circuit:

 

Ans;

```
module top_module (
    input clk,
    input in,
    output out);
    always @ (posedge clk) begin
        out <= out ^ in;
    end
endmodule
```

 92. Consider the sequential circuit below:




Assume that you want to implement hierarchical Verilog code for this circuit, using three instantiations of a submodule that has a flip-flop and multiplexer in it. Write a Verilog module (containing one flip-flop and multiplexer) named top_module for this submodule.

Ans;

```
module top_module (
    input clk,
```

 
93. Consider the n-bit shift register circuit shown below:



```
module top_module (
```

```
input clk,  
input w, R, E, L,  
output Q  
);  
  
wire [1:0] con;  
assign con = {E,L};  
  
always @ (posedge clk) begin
```

```

case (con)

    2'b00 : Q <= Q;

    2'b01 : Q <= R;

                2'b10 : Q <= w;

    2'b11 : Q <= R;

endcase


end

endmodule

```

94. Given the finite state machine circuit as shown, assume that the D flip-flops are initially reset to zero before the machine begins.

Build this circuit.

 


Ans;

```

module top_module (
    input clk,
    input x,
    output z
);
    reg [2:0] Q;
    always@(posedge clk)begin
        Q[0] <= Q[0] ^ x;
        Q[1] <= ~Q[1] & x;
        Q[2] <= ~Q[2] | x;
    end
    assign z = ~(| Q);
endmodule

```

 

95. A JK flip-flop has the below truth table. Implement a JK flip-flop with only a D-type flip-flop and gates. Note: Qold is the output of the D flip-flop before the positive clock edge.


J	K	Q
0	0	Qold
0	1	0
1	0	1
1	1	$\sim Qold$

Ans;

```


module top_module (
    input clk,
    input j,
    input k,
    output Q);
    always @(posedge clk) begin
        case({j, k})
            2'b00 : Q <= Q;
            2'b01 : Q <= 0;
            2'b10 : Q <= 1;
            2'b11 : Q <= ~Q;
        endcase
    end
endmodule

```

 

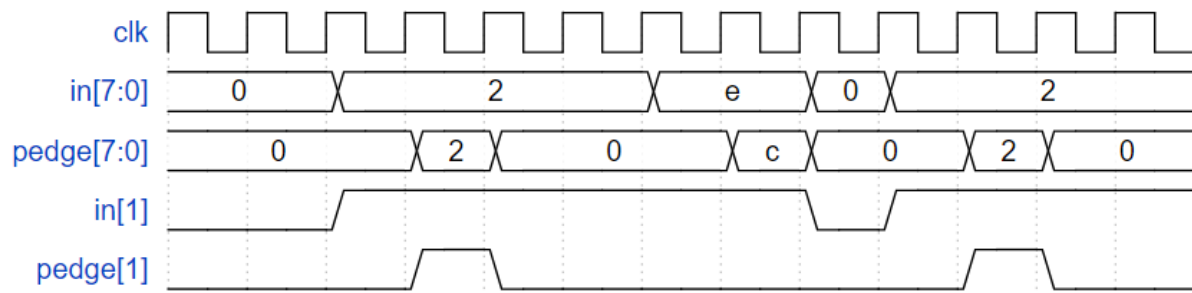96. For each bit in an 8-bit vector, detect when the input signal changes from 0 in one clock cycle to 1 the next (similar to positive edge detection). The output bit should be set the cycle after a 0 to 1 transition occurs.

Here are some examples. For clarity, in[1] and pedge[1] are shown separately.



Ans;

```
module top_module (
    input clk,
    input [7:0] in,
    output [7:0] pedge
);
```

```
    reg [7:0] intermediate;
```


```
    always @ (posedge clk) begin
```

```
        intermediate <= in;
```

```
        pedge <= (~intermediate) & in;
```


```
    end
```

```
endmodule
```

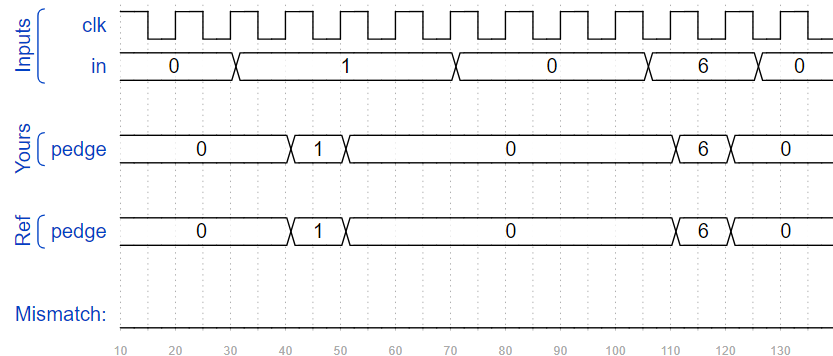

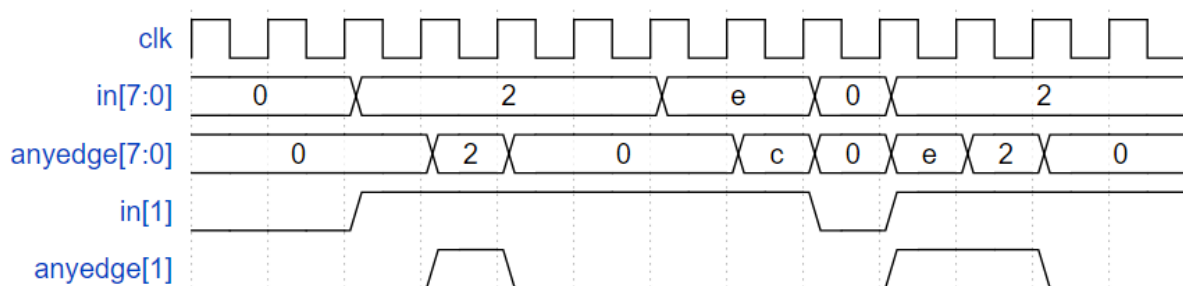97. For each bit in an 8-bit vector, detect when the input signal changes from one clock cycle to the next (detect any edge). The output bit should be set the cycle after a 0 to 1 transition occurs.

Here are some examples. For clarity, in[1] and anyedge[1] are shown separately



Ans;


```
module top_module (
```

```
    input clk,
```

```

input [7:0] in,
output [7:0] anyedge
);
    reg [7:0] intermediate;
    always @ (posedge clk) begin
        intermediate <= in;
        anyedge    <= intermediate ^ in;
    end
endmodule


```

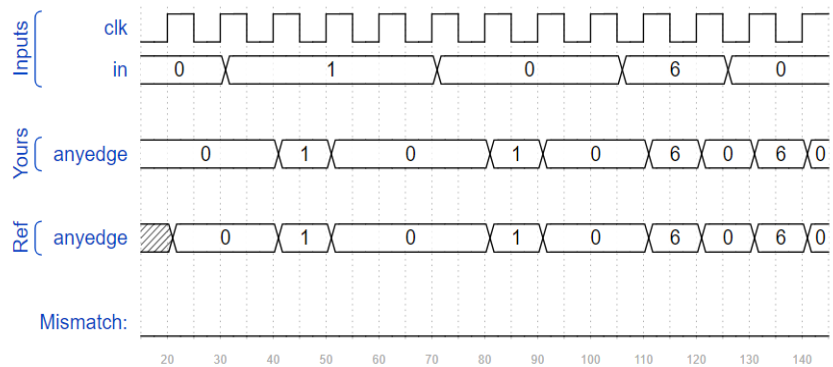

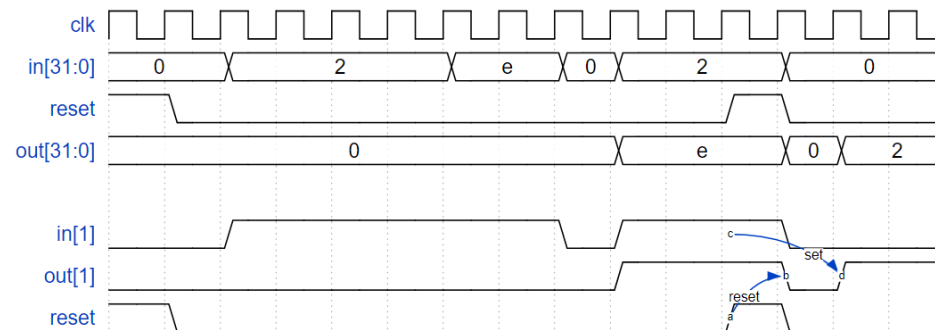98. For each bit in a 32-bit vector, capture when the input signal changes from 1 in one clock cycle to 0 the next. "Capture" means that the output will remain 1 until the register is reset (synchronous reset).

Each output bit behaves like a SR flip-flop: The output bit should be set (to 1) the cycle after a 1 to 0 transition occurs. The output bit should be reset (to 0) at the positive clock edge when reset is high. If both of the above events occur at the same time, reset has precedence. In the last 4 cycles of the example waveform below, the 'reset' event occurs one cycle earlier than the 'set' event, so there is no conflict here.

In the example waveform below, reset, in[1] and out[1] are shown again separately for clarity.



Ans;

```

module top_module (
    input clk,
    input reset,
    input [31:0] in,
    output [31:0] out
);

```

```
reg [31:0] in_last; //the input in last clk
```

```
always @(posedge clk) begin
```

```
    in_last <= in;
```

```
    if(reset) out <= 0;
```



```
    else begin
```

```
        out <= out | (in_last & ~in);
```


```
    end
```

```
end
```

```
endmodule
```

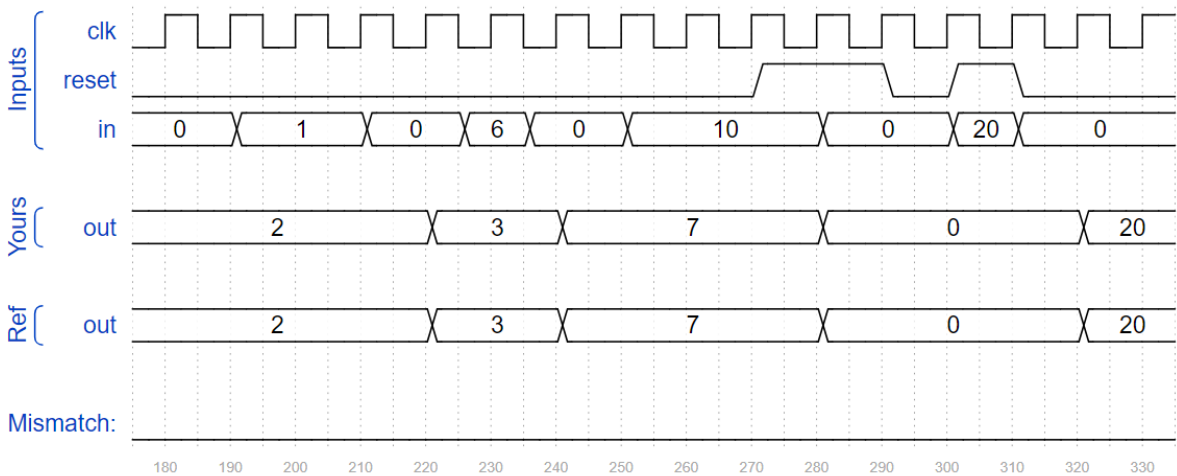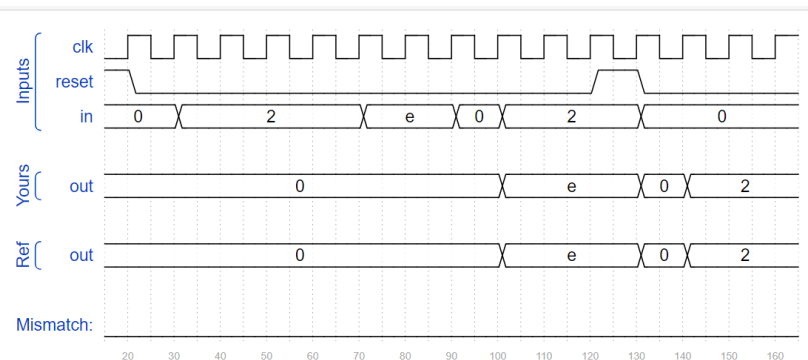

 99. Build a circuit that functionally behaves like a dual-edge triggered flip-flop:



Ans;

```
module top_module (
```

```
    input clk,
```


```
    input d,
```

```
    output q
```

```
);
```

```
reg q1,q2;
```

```
always @ (posedge clk) begin
```

 


```

        q1 <= q2^d;
    end
    always @ (negedge clk) begin
        q2 <= q1^d;
    end
    assign q = q1^q2;
endmodule

```

 100. Build a 4-bit binary counter that counts from 0 through 15, inclusive, with a period of 16. The reset input is synchronous, and should reset the counter to 0.




Ans;


```

module top_module (
    input clk,
    input reset,
    output [3:0] q);
    always @ (posedge clk) begin
        if (reset) q <= 4'd0;
        else q <= q+4'd1;
    end
endmodule

```

 

 101. Build a decade counter that counts from 0 through 9, inclusive, with a period of 10. The reset input is synchronous, and should reset the counter to 0.




Ans;

```

module top_module (
    input clk,

```

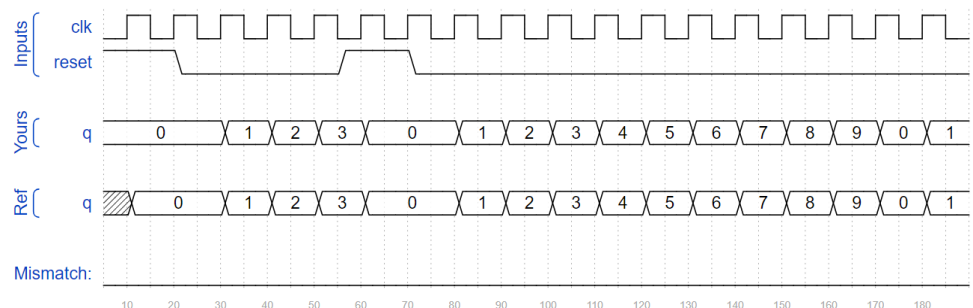


```

input reset,
output [3:0] q;
always @ (posedge clk) begin
    if (reset) q <= 4'd0;
    else if (q == 4'd9) q<= 4'd0;
    else q <= q+4'd1;
end
endmodule

```

 102. Make a decade counter that counts 1 through 10, inclusive. The reset input is synchronous, and should reset the counter to 1.



Ans;

```

module top_module (

```

```

    input clk,
    input reset,
    output [3:0] q;

```

```

always @ (posedge clk) begin

```

```

    if (reset) q <= 4'd1;
    else if (q == 4'd10) q<= 4'd1;
    else q <= q+4'd1;

```

```


end

```

```


endmodule

```

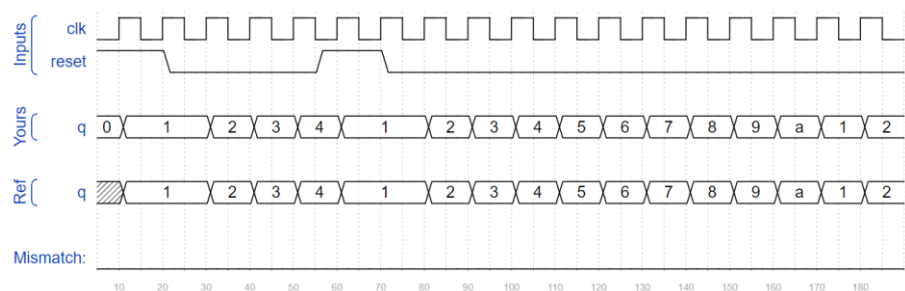

 103. Build a decade counter that counts from 0 through 9, inclusive, with a period of 10. The reset input is synchronous, and should reset the counter to 0. We want to be able to pause the counter rather than always incrementing every clock cycle, so the slowena input

indicates when the counter should increment.



Ans;

```
module top_module (
```

```
    input clk,
```

```
    input slowena,
```

```
    input reset,
```

```
    output [3:0] q);
```

```
    always @ (posedge clk) begin
```

```
        if (reset) q <= 4'd0;
```

```
        else if (slowena) begin
```


```
            if (q == 4'd9) q <= 4'd0;
```

```
            else q <= q+4'd1;
```

```
        end
```


```
    end
```

```
endmodule
```

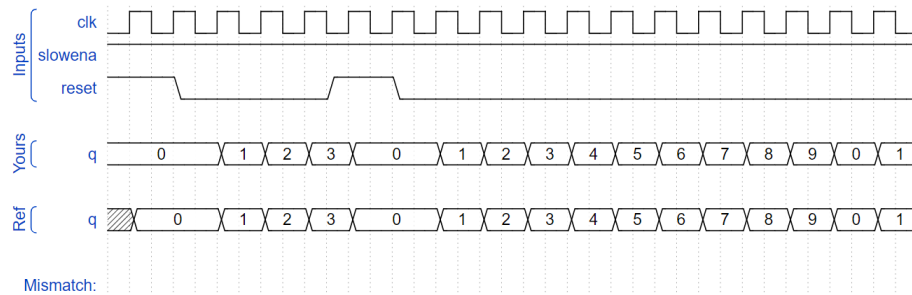

Synchronous reset and counting.

Enable/disable

 

104. Design a 1-12 counter with the following inputs and outputs:

Reset Synchronous active-high reset that forces the counter to 1

Enable Set high for the counter to run

Clk Positive edge-triggered clock input

Q[3:0] The output of the counter

c_enable, c_load, c_d[3:0] Control signals going to the provided 4-bit counter, so correct operation can be verified.

You have the following components available:

the 4-bit binary counter (count4) below, which has Enable and synchronous parallel-load inputs (load has higher priority than enable). The count4 module is provided to you.

Instantiate it in your circuit.

logic gates

```

module count4(
    input clk,
    input enable,
    input load,
    input [3:0] d,
    output reg [3:0] Q
);

```


The `c_enable`, `c_load`, and `c_d` outputs are the signals that go to the internal counter's enable, load, and d inputs, respectively. Their purpose is to allow these signals to be checked for correctness.

Ans;

```

module top_module (
    input clk,
    input reset,
    input enable,
    output [3:0] Q,
    output c_enable,
    output c_load,
    output [3:0] c_d
);

```

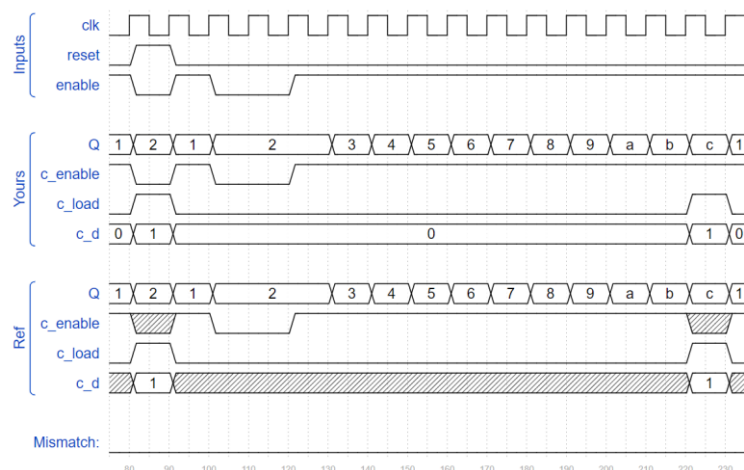

```

);

    initial Q <= 1;

    always @(posedge clk) begin
        if(reset | ((Q == 12) & enable)) Q <= 1;
        else Q <= (enable) ? Q + 1 : Q;
    end

    assign c_enable = enable;
    assign c_load = (reset | ((Q == 12) & enable));
    assign c_d = c_load ? 1 : 0;
    count4 the_counter (clk, c_enable, c_load, c_d /*, ... */);
endmodule

```

105. From a 1000 Hz clock, derive a 1 Hz signal, called OneHertz, that could be used to drive an Enable signal for a set of hour/minute/second counters to create a digital wall clock. Since we want the clock to count once per second, the OneHertz signal must be asserted for exactly one cycle each second. Build the frequency divider using modulo-10 (BCD) counters and as few other gates as possible. Also output the enable signals from each of the BCD counters you use (c_enable[0] for the fastest counter, c_enable[2] for the slowest).

The following BCD counter is provided for you. Enable must be high for the counter to run. Reset is synchronous and set high to force the counter to zero. All counters in your circuit must directly use the same 1000 Hz signal.

```
module bcdcount (
    input clk,
    input reset,
    input enable,
    output reg [3:0] Q);
```

```
ans;
```

```
module top_module (
```

```
    input clk,
```

```
    input reset,
```

```
    output OneHertz,
```

```
    output [2:0] c_enable
```

```
);
```

```
    wire [3:0] q0, q1, q2;
```

```
    bcdcount counter0 (clk, reset, c_enable[0], q0);
```


```
    bcdcount counter1 (clk, reset, c_enable[1], q1);
```

```
    bcdcount counter2 (clk, reset, c_enable[2], q2);
```

```
    assign c_enable = {(q1 == 4'd9) & (q0 == 4'd9), q0 == 4'd9, 1'b1};
```


```
    assign OneHertz = (q2 == 4'd9) & (q1 == 4'd9) & (q0 == 4'd9);
```

```
endmodule
```

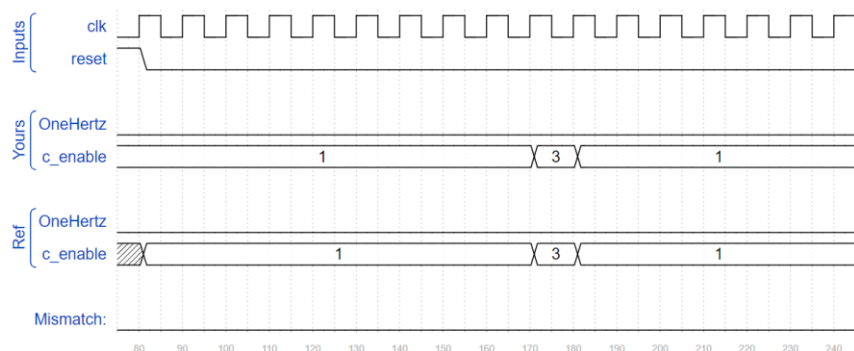


Basic counting


Roll-over at count 90 and 100

 

Roll-over at count 990 and 1000

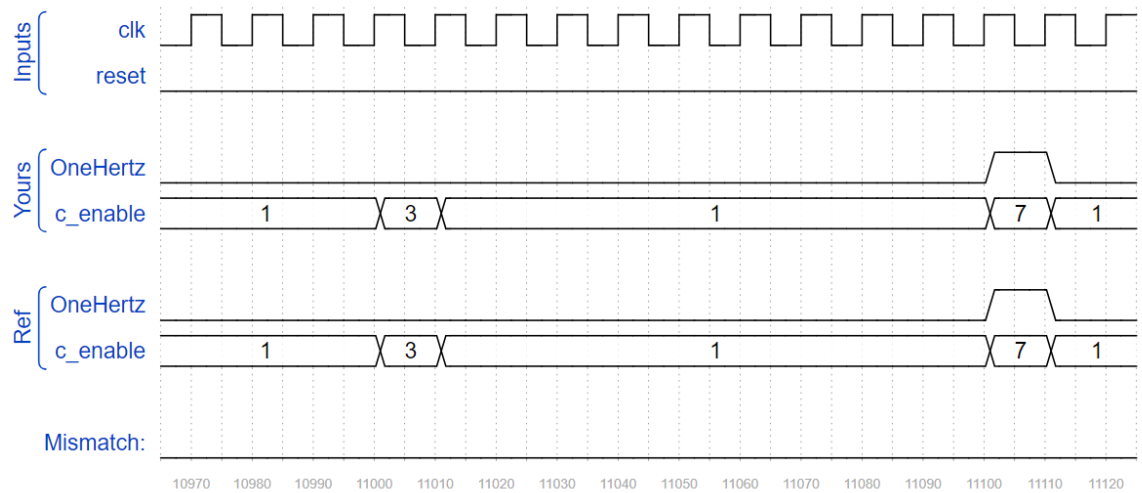

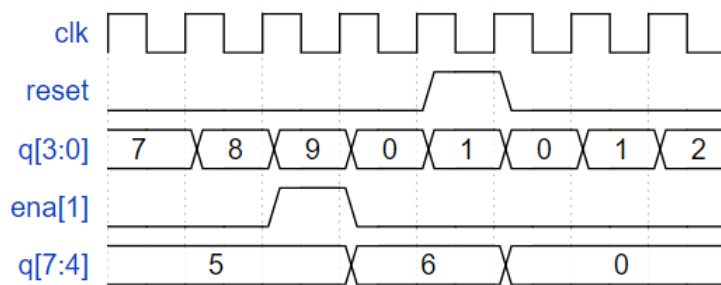106. Build a 4-digit BCD (binary-coded decimal) counter. Each decimal digit is encoded using 4 bits: $q[3:0]$ is the ones digit, $q[7:4]$ is the tens digit, etc. For digits [3:1], also output an enable signal indicating when each of the upper three digits should be incremented.



Ans;

```
module top_module (
```

```
    input clk,
```

```

input reset, // Synchronous active-high reset
output [3:1] ena,
output [15:0] q);

assign ena = {q[11:8] == 4'd9 && q[7:4] == 4'd9 && q[3:0] == 4'd9, q[7:4] == 4'd9 &&
q[3:0] == 4'd9, q[3:0] == 4'd9};

count4 inst1_count4
(
    .clk(clk),
    .reset(reset),
    .ena(1),
    .q(q[3:0])
);

count4 inst2_count4
(
    .clk(clk),
    .reset(reset),
    .ena(ena[1]),
    .q(q[7:4])
);

count4 inst3_count4
(
    .clk(clk),
    .reset(reset),
    .ena(ena[2]),
    .q(q[11:8])
);

count4 inst4_count4
(
    .clk(clk),
    .reset(reset),

```



```

        .ena(ena[3]),
        .q(q[15:12])
    );
endmodule

module count4
    (
        input clk,
        input reset,
        input ena,
        output reg[3:0] q
    );
    always @(posedge clk) begin
        if(reset) q <= 4'd0;
        else begin
            if(ena) begin
                if(q == 4'd9) q <= 4'd0;
                else q <= q + 1;
            end
        end
    end
endmodule

```


Counting

 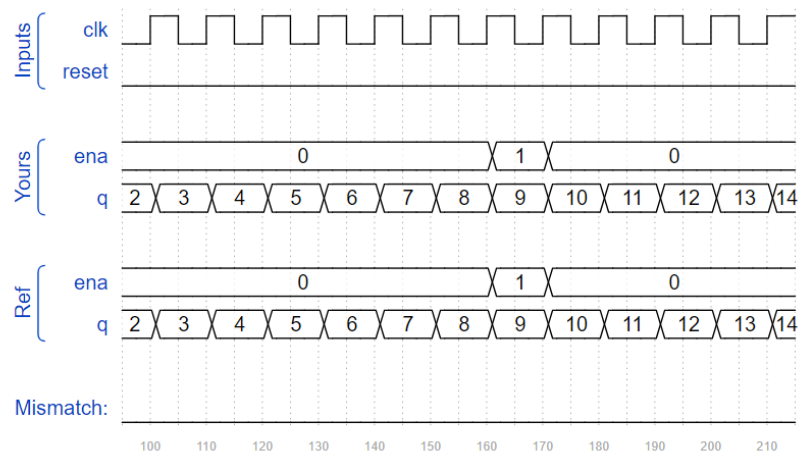

 107. Create a set of counters suitable for use as a 12-hour clock (with am/pm indicator). Your counters are clocked by a fast-running `clk`, with a pulse on `ena` whenever your clock should increment (i.e., once per second).

`reset` resets the clock to 12:00 AM. `pm` is 0 for AM and 1 for PM. `hh`, `mm`, and `ss` are two BCD (Binary-Coded Decimal) digits each for hours (01-12), minutes (00-59), and seconds (00-59). Reset has higher priority than enable, and can occur even when not enabled.

The following timing diagram shows the rollover behaviour from 11:59:59 AM to 12:00:00 PM and the synchronous reset and enable behaviour.



Ans;

```
module top_module(
```

```
    input clk,
```

```
    input reset,
```

```
    input ena,
```


```
    output pm,
```

```
    output [7:0] hh,
```

```
    output [7:0] mm,
```

```
    output [7:0] ss);
```

Reset and count to 10

 

```
reg [2:0] ena_hms; //determine when will "ss","mm" and "hh" need to be increased
```

```
assign ena_hms = {(ena && (mm == 8'h59) && (ss == 8'h59)), (ena && (ss == 8'h59)), ena};
```

Minute roll-over

```
count60 count_ss(
```

```
    .clk(clk),
```

```
    .reset(reset),
```

```
    .ena(ena_hms[0]),
```

```
    .q(ss)
```


```
);
```

```
count60 count_mm(
```

```
    .clk(clk),
```

```
    .reset(reset),
```

```
    .ena(ena_hms[1]),
```

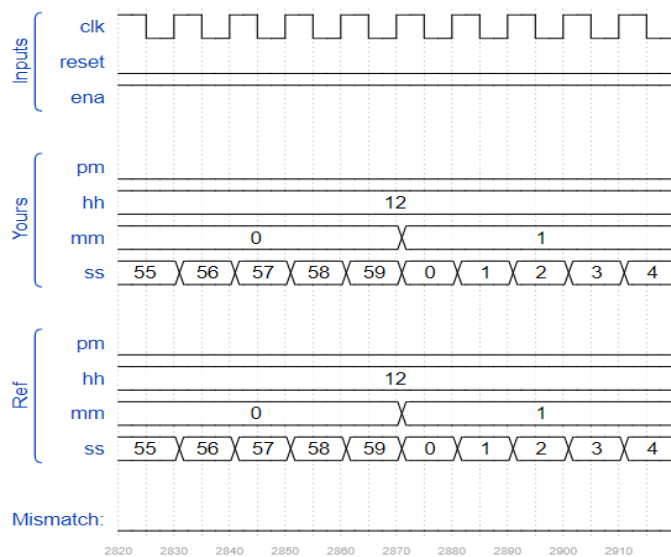

```

.q(mm)
);

always @(posedge clk) begin
    if(reset) begin
        hh <= 8'h12; //hh=12
        pm <= 0;
    end
    else begin

```

```

        if(ena_hms[2]) begin //if mm=59 and ss=59
            if(hh == 8'h12) hh <= 8'h1; //hh will change:12AM->1AM or 12PM->1PM
            else if(hh == 8'h11) begin //if hh=11, then PM->AM or AM->PM
                hh[3:0] <= hh[3:0] + 1'h1; //hh=12
                pm <= ~pm;
            end
        end
    end
    else begin

```

```

        if(hh[3:0] == 4'h9) begin
            hh[3:0] <= 4'h0;
            hh[7:4] <= hh[7:4] + 1'h1;
        end
        else hh[3:0] = hh[3:0] + 1'h1;
    end
end
else hh <= hh;
end
end


```

```


endmodule

```

Hour roll-over

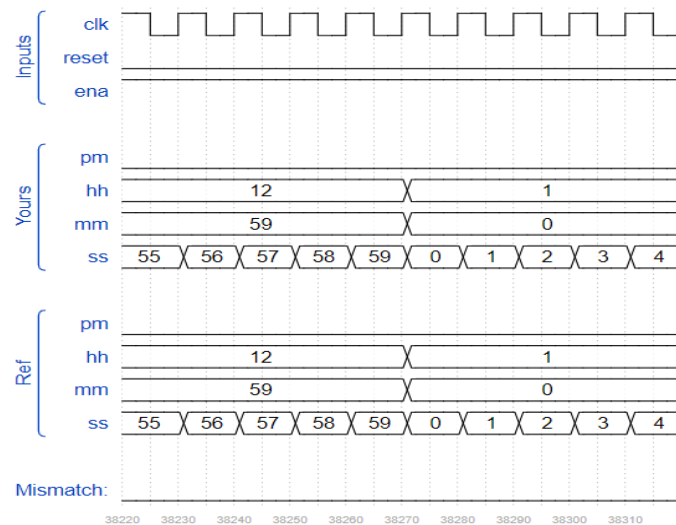

PM roll-over

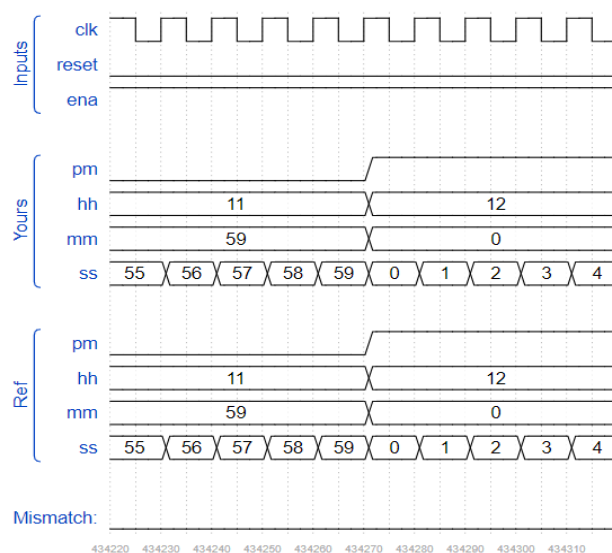


```

module count60(
    input clk,
    input reset,
    input ena,
    output [7:0] q
);
always @(posedge clk) begin
    if(reset) q <= 8'h0;
    else begin
        if(ena) begin
            if(q[3:0] == 4'h9) begin
                if(q[7:4] == 4'h5) q <= 8'h0;
                else begin
                    q[7:4] <= q[7:4] + 1'h1;
                    q[3:0] <= 4'h0;
                end
            end
            else q[3:0] <= q[3:0] + 1'h1;
        end
        else q <= q;
    end
end
endmodule

```

108. Build a 4-bit shift register (right shift), with asynchronous reset, synchronous load, and enable.

areset: Resets shift register to zero.

load: Loads shift register with data[3:0] instead of shifting.

ena: Shift right (q[3] becomes zero, q[0] is shifted out and disappears).

q: The contents of the shift register.

If both the load and ena inputs are asserted (1), the load input has higher priority.

Ans;

```
module top_module(
```

```
    input clk,
```

```
    input areset,
```

```
    input load,
```

```
    input ena,
```

```
    input [3:0] data,
```

```
    output reg [3:0] q);
```

```
    always @(posedge clk or posedge areset) begin
```

```
        if(areset) begin
```

```
            q <= 0;
```

```
        end
```

```
        else begin
```

```
            if(load) begin
```

```
                q <= data;
```

```
            end
```

```
            else begin
```

```
                if(ena) begin
```

```
                    q <= (q >> 1);
```

```
                end
```


```
            end
```

```
        end
```

```
    end
```

```
endmodule
```

Load and reset

 

109. Build a 100-bit left/right rotator, with synchronous load and left/right enable. A rotator shifts-in the shifted-out bit from the other end of the register, unlike a shifter that discards the shifted-out bit and shifts in a zero. If enabled, a rotator rotates the bits around and does not modify/discard them.

load: Loads shift register with data[99:0] instead of rotating.

ena[1:0]: Chooses whether and which direction to rotate.

2'b01 rotates right by one bit

2'b10 rotates left by one bit

2'b00 and 2'b11 do not rotate.

q: The contents of the rotator.

Ans;

```
module top_module(  
    input clk,  
    input load,  
    input [1:0] ena,  
    input [99:0] data,  
    output reg [99:0] q);  
    always @(posedge clk) begin  
        if(load) q <= data;  
        else begin  
            if(ena == 2'b01) q <= {q[0], q[99:1]};  
            else if(ena == 2'b10) q <= {q[98:0], q[99]};  
            else q <= q;  
        end  
    end  
endmodule
```

110. Build a 64-bit arithmetic shift register, with synchronous load. The shifter can shift both left and right, and by 1 or 8 bit positions, selected by amount.

An arithmetic right shift shifts in the sign bit of the number in the shift register (q[63] in this case) instead of zero as done by a logical right shift. Another way of thinking about an arithmetic right shift is that it assumes the number being shifted is signed and preserves the sign, so that arithmetic right shift divides a signed number by a power of two.

There is no difference between logical and arithmetic left shifts.

load: Loads shift register with data[63:0] instead of shifting.

ena: Chooses whether to shift.

amount: Chooses which direction and how much to shift.

2'b00: shift left by 1 bit.

2'b01: shift left by 8 bits.

2'b10: shift right by 1 bit.

2'b11: shift right by 8 bits.

q: The contents of the shifter.

Ans;

```
module top_module(  
    input clk,  
    input load,  
    input ena,  
    input [1:0] amount,  
    input [63:0] data,  
    output reg [63:0] q);
```

```
    always @(posedge clk) begin
```

```
        if(load) q <= data;
```

```
        else begin
```

```
            if(ena) begin
```

```
                if(amount == 2'b00) q <= (q << 1);
```

```
                else if(amount == 2'b01) q <= (q << 8);
```

```
                else if(amount == 2'b10) begin
```

```
                    if(q[63] == 0) q <= (q >> 1);
```


```
                    else begin
```

```
                        q <= (q >> 1);
```

```
                        q[63] <= 1'b1;
```

```
                    end
```

```
                end
```

 

```

else begin
    if(q[63] == 0) q <= (q >> 8);
    else begin
        q <= (q >> 8);
        q[63:56] <= {8{1'b1}};
    end
end

end


end

end

endmodule

```

 111. The following diagram shows a 5-bit maximal-length Galois LFSR with taps at bit positions 5 and 3. (Tap positions are usually numbered starting from 1). Note that I drew the XOR gate at position 5 for consistency, but one of the XOR gate inputs is 0.



Ans;

```

module top_module(

```

```

    input clk,

```

```

    input reset,

```

```

    output [4:0] q

```

```

);

```

```

    always @(posedge clk) begin

```

```

        if(reset) q <= 5'h1;

```

```

        else q <= {q[0]^1'b0, q[4], q[3]^q[0], q[2], q[1]};

```

```


    end

```


```

endmodule

```

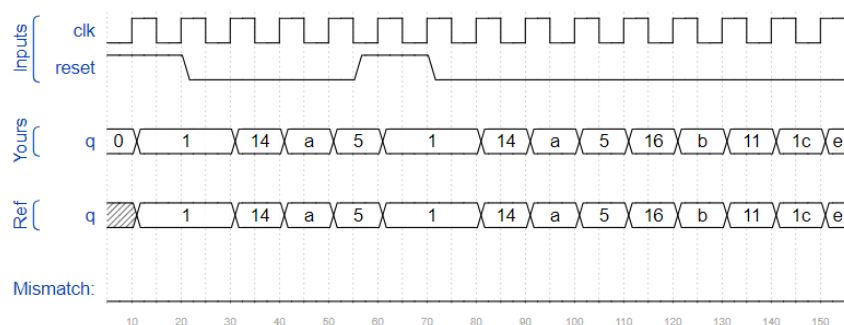

 112. Write the Verilog code for this sequential circuit (Submodules are ok, but the top-level must be named top_module). Assume that you are going to implement the circuit on the DE1-SoC board. Connect the R inputs to the SW switches, connect Clock to KEY[0], and L to KEY[1]. Connect the Q outputs to the red lights LEDR.



Ans;

```
module top_module (
    input [2:0] SW,
    input [1:0] KEY,
    output [2:0] LEDR);

    wire L;
    wire clk;
    wire [2:0] R;
    reg [2:0] Q;

    assign R = SW;
    assign clk = KEY[0];
    assign L = KEY[1];

    always @(posedge clk) begin
        if(L) Q <= R;
        else Q <= {Q[2]^Q[1], Q[0], Q[2]};
    end

    assign LEDR = Q;
endmodule
```

113. Build a 32-bit Galois LFSR with taps at bit positions 32, 22, 2, and 1.


Ans;

```

module top_module(
    input clk,
    input reset,
    output [31:0] q
);
    always @(posedge clk) begin
        if(reset) q <= 32'h1;
        else begin
            q <= {0^q[0], q[31:23], q[22]^q[0], q[21:3], q[2]^q[0], q[1]^q[0]};
        end
    end
endmodule

```

114. Implement the following circuit:

 

Ans;

```

module top_module (
    input clk,
    input resetrn,
    input in,
    output out);
    reg [2:0] Q;
    always @(posedge clk) begin


```

```

if(resetn) begin
    Q[0] <= in;
    Q[1] <= Q[0];
    Q[2] <= Q[1];
    out <= Q[2];
end
else begin
    Q <= 3'b0;
    out <= 1'b0;
end
end
endmodule

```

 115. Consider the n-bit shift register circuit shown below:



Ans;

```

module top_module (
    input [3:0] SW,
    input [3:0] KEY,
    output [3:0] LEDR
);
    MUXDFF ins0(SW[3], KEY[0], KEY[1], KEY[2], KEY[3], LEDR[3]);
    MUXDFF ins1(SW[2], KEY[0], KEY[1], KEY[2], LEDR[3], LEDR[2]);
    MUXDFF ins2(SW[1], KEY[0], KEY[1], KEY[2], LEDR[2], LEDR[1]);

```



```

    MUXDFF ins3(SW[0], KEY[0], KEY[1], KEY[2], LEDR[1], LEDR[0]);
endmodule

module MUXDFF (
    input R,
    input clk,
    input E,
    input L,
    input w,
    output out
);
    wire [1:0] temp;
    assign temp[0] = E ? w : out;
    assign temp[1] = L ? R : temp[0];
    always @(posedge clk) begin
        out <= temp[1];
    end
endmodule

```

116. In this question, you will design a circuit for an 8x1 memory, where writing to the memory is accomplished by shifting-in bits, and reading is "random access", as in a typical RAM. You will then use the circuit to realize a 3-input logic function.

First, create an 8-bit shift register with 8 D-type flip-flops. Label the flip-flop outputs from Q[0]...Q[7]. The shift register input should be called S, which feeds the input of Q[0] (MSB is shifted in first). The enable input controls whether to shift. Then, extend the circuit to have 3 additional inputs A,B,C and an output Z. The circuit's behaviour should be as follows: when ABC is 000, Z=Q[0], when ABC is 001, Z=Q[1], and so on. Your circuit should contain ONLY the 8-bit shift register, and multiplexers. (Aside: this circuit is called a 3-input look-up-table (LUT)).

Ans;

```

module top_module (
    input clk,
    input enable,
    input S,

```

input A, B, C,

output Z);

reg[7:0] q;

always @(posedge clk) begin

if(enable) begin

q <= {q[6:0], S}; //q[7]=q[6], q[6]=q[5]...q[0]=S

end

else q <= q;

end

always @(*) begin

case({A, B, C})

3'b000 : Z = q[0];

3'b001 : Z = q[1];

3'b010 : Z = q[2];

3'b011 : Z = q[3];

3'b100 : Z = q[4];

3'b101 : Z = q[5];


3'b110 : Z = q[6];

3'b111 : Z = q[7];

endcase

end

endmodule

 


117. In this circuit, create a 512-cell system ($q[511:0]$), and advance by one time step each clock cycle. The load input indicates the state of the system should be loaded with $data[511:0]$. Assume the boundaries ($q[-1]$ and $q[512]$) are both zero (off).

Left	Center	Right	Center's next state
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	1
0	1	1	1
0	1	0	0
0	0	1	1
0	0	0	0

Ans;
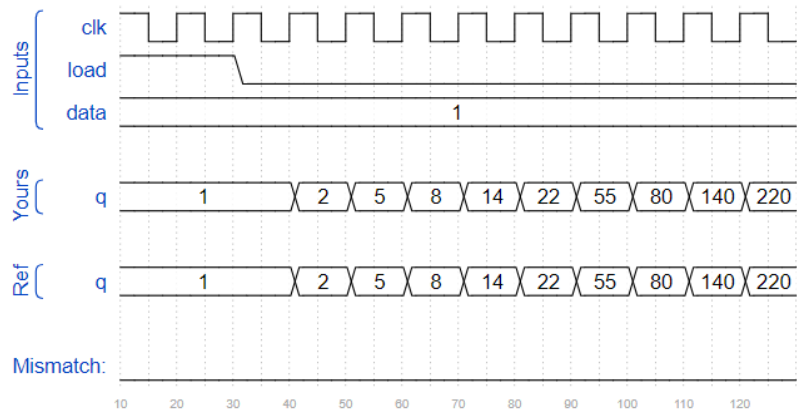
```
module top_module(
    input clk,
    input load,
    input [511:0] data,
    output [511:0] q );
    always@(posedge clk) begin
        if(load) q <= data;
        else q <= {1'b0, q[511:1]} ^ {q[510:0], 1'b0};
    end
endmodule
```




118. There is a one-dimensional array of cells (on or off). At each time step, the state of each cell changes. In Rule 110, the next state of each cell depends only on itself and its two neighbours, according to the following table:

Left	Center	Right	Center's next state
1	1	1	0
1	1	0	1
1	0	1	1
1	0	0	0
0	1	1	1
0	1	0	1
0	0	1	1
0	0	0	0

In this circuit, create a 512-cell system (q[511:0]), and advance by one time step each clock cycle. The load input indicates the state of the system should be loaded with data[511:0]. Assume the boundaries (q[-1] and q[512]) are both zero (off).

Ans;
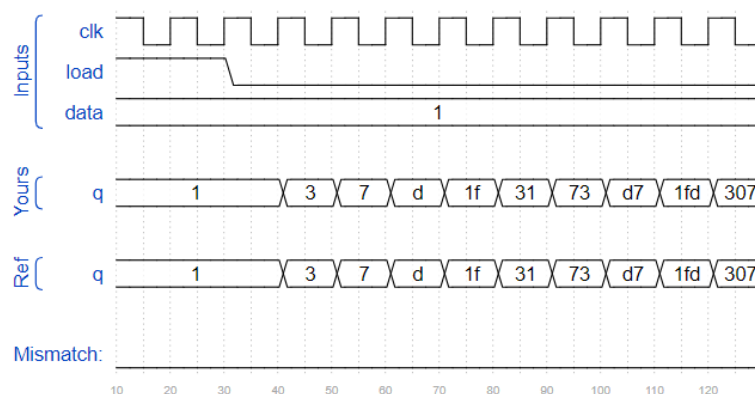
```
module top_module(
    input clk,
    input load,
    input [511:0] data,
    output [511:0] q
);
```



```

always @(posedge clk) begin
    if (load) begin
        q <= data;
    end
    else begin
        q <= (((q[511:0] ^ {q[510:0], 1'b0}) & q[511:1]) | ((q[511:0] | {q[510:0],
1'b0}) & (~q[511:1])));
    end
end
endmodule

```

119. The "game" is played on a two-dimensional grid of cells, where each cell is either 1 (alive) or 0 (dead). At each time step, each cell changes state depending on how many neighbours it has:

0-1 neighbour: Cell becomes 0.

2 neighbours: Cell state does not change.

3 neighbours: Cell becomes 1.

4+ neighbours: Cell becomes 0.

The game is formulated for an infinite grid. In this circuit, we will use a 16x16 grid. To make things more interesting, we will use a 16x16 toroid, where the sides wrap around to the other side of the grid. For example, the corner cell (0,0) has 8 neighbours: (15,1), (15,0), (15,15), (0,1), (0,15), (1,1), (1,0), and (1,15). The 16x16 grid is represented by a length 256 vector, where each row of 16 cells is represented by a sub-vector: q[15:0] is row 0, q[31:16] is row 1, etc. (This tool accepts SystemVerilog, so you may use 2D vectors if you wish.)

load: Loads data into q at the next clock edge, for loading initial state.

q: The 16x16 current state of the game, updated every clock cycle.

The game state should advance by one timestep every clock cycle.

Ans; module top_module(

input clk,

input load,

input [255:0] data,

output [255:0] q);

reg [255:0] q_next;

```

reg [3:0] sum;

always@(posedge clk) begin

    if(load)

        q <= data;

    else begin

        for(int i=0; i<256; i++) begin

            if(i == 0)

                sum = q[1] + q[16] + q[17] + q[240] + q[241] + q[15] + q[31] + q[255];

            else if(i == 15)

                sum = q[14] + q[16] + q[0] + q[240] + q[254] + q[30] + q[31] + q[255];

            else if(i == 240)

                sum = q[0] + q[15] + q[239] + q[241] + q[1] + q[224] + q[225] + q[255];

            else if(i == 255)

                sum = q[0] + q[15] + q[14] + q[224] + q[238] + q[240] + q[239] + q[254];

            else if(0<i & i<15)

                sum = q[i-1] + q[i+1] + q[i+15] + q[i+16] + q[i+17] + q[i+239] + q[i+240] + q[i+241];

            else if(i%16 == 0)

                sum = q[i-1] + q[i+1] + q[i+15] + q[i+16] + q[i+17] + q[i-16] + q[i-15] + q[i+31];

            else if(i%16 == 15)

                sum = q[i-1] + q[i+1] + q[i+15] + q[i+16] + q[i-17] + q[i-16] + q[i-15] + q[i-31];

            else if(240<i & i<255)

                sum = q[i-1] + q[i+1] + q[i-17] + q[i-16] + q[i-15] + q[i-239] + q[i-240] + q[i-241];

            else

                sum = q[i-1] + q[i+1] + q[i-17] + q[i-16] + q[i-15] + q[i+15] + q[i+16] + q[i+17];

            case(sum)

                2:q_next[i] = q[i];

                3:q_next[i] = 1;

                default:q_next[i] = 0;

            endcase

        end

    end

```


```

        end
        q = q_next;
    end
end
endmodule

```

 120. This is a Moore state machine with two states, one input, and one output. Implement this state machine. Notice that the reset state is B.

This exercise is the same as fsm1s, but using asynchronous reset.



Ans;

```

module top_module(
    input clk,
    input areset, // Asynchronous reset to state B
    input in,
    output out);

    parameter A=0, B=1;
    reg state, next_state;

    always @(*) begin // This is a combinational always block
        // State transition logic
        case(state)
            A : next_state = (in == 1) ? A : B;
            B : next_state = (in == 1) ? B : A;
        endcase
    end
end

```

```
always @(posedge clk, posedge areset) begin // This is a sequential always block
```

```
// State flip-flops with asynchronous reset
```


```
if(areset) state <= B;
```

```
else state <= next_state;
```

```
end
```

```
// Output logic
```


```
assign out = (state == B);
```

 

```
endmodule
```

 121. This is a Moore state machine with two states, one input, and one output. Implement this state machine. Notice that the reset state is B.

This exercise is the same as fsm1, but using synchronous reset.



Ans;

// Note the Verilog-1995 module declaration syntax here:

```
module top_module(clk, reset, in, out);
```

```
input clk;
```

```
input reset; // Synchronous reset to state B
```

```
input in;
```

```
output out; //
```

```
// Fill in state name declarations
```

```
parameter A = 0, B = 1;
```

```
reg present_state, next_state;
```

```
always @(posedge clk) begin
```

```
if (reset) present_state <= B;
```

```
else present_state <= next_state;
```

```


end

always @(*) begin
    case (present_state)
        B : next_state <= (in == 1) ? B : A;
        A : next_state <= (in == 1) ? A : B;
    endcase
end

assign out = (present_state == B);


endmodule

```

 

 122. This is a Moore state machine with two states, two inputs, and one output. Implement this state machine.

This exercise is the same as fsm2s, but using asynchronous reset.




Ans;

```

module top_module(
    input clk,
    input areset, // Asynchronous reset to OFF
    input j,
    input k,
    output out); //
    parameter OFF=0, ON=1;
    reg state, next_state;
    always @(*) begin
        case(state)
            OFF:next_state=(j==1)?ON:OFF;
            ON:next_state=(k==1)?OFF:ON;
        endcase
    end

```

 


```

end

always @(posedge clk, posedge areset) begin

    if(areset)state<=OFF;

    else state<=next_state;

end

// Output logic


assign out = (state == ON);

endmodule

```

 123. This is a Moore state machine with two states, two inputs, and one output. Implement this state machine.

This exercise is the same as fsm2, but using synchronous reset.



Ans;

```

module top_module(
    input clk,
    input reset, // Synchronous reset to OFF
    input j,
    input k,
    output out); //
    parameter OFF=0, ON=1;
    reg state, next_state;
    always @(*) begin
        case(state)
            OFF:next_state=(j==0)?OFF:ON;
            ON:next_state=(k==0)?ON:OFF;
        endcase
    end
    // State transition logic

```

```

end

always @(posedge clk) begin

    if(reset)state<=OFF;


    else state<=next_state;

end

// Output logic

assign out = (state == ON);

```

 

endmodule

124. The following is the state transition table for a Moore state machine with one input, one output, and four states. Use the following state encoding: A=2'b00, B=2'b01, C=2'b10, D=2'b11.

Implement only the state transition logic and output logic (the combinational logic portion) for this state machine. Given the current state (state), compute the next_state and output (out) based on the state transition table.

State	Next state		Output
	in=0	in=1	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

Ans;

```

module top_module(
    input in,
    input [1:0] state,
    output [1:0] next_state,
    output out); //

parameter A=0, B=1, C=2, D=3;

always@(*)begin

    case(state)

        A:next_state=(in==0)?A:B;

        B:next_state=(in==0)?C:B;

```

```

        C:next_state=(in==0)?A:D;

        D:next_state=(in==0)?C:B;

    endcase

end

assign out=(state==D);

endmodule

```

125. The following is the state transition table for a Moore state machine with one input, one output, and four states. Use the following one-hot state encoding: A=4'b0001, B=4'b0010, C=4'b0100, D=4'b1000.

Derive state transition and output logic equations by inspection assuming a one-hot encoding. Implement only the state transition logic and output logic (the combinational logic portion) for this state machine. (The testbench will test with non-one hot inputs to make sure you're not trying to do something more complicated).

State	Next state		Output
	in=0	in=1	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

Ans;

```

module top_module(
    input in,
    input [3:0] state,
    output [3:0] next_state,
    output out);

    parameter A=0, B=1, C=2, D=3;

    assign next_state[A] = (state[A] & ~in) | (state[C] & ~in);
    assign next_state[B] = (state[A] & in) | (state[B] & in) | (state[D] & in);
    assign next_state[C] = (state[B] & ~in) | (state[D] & ~in);
    assign next_state[D] = state[C] & in;

```

```
assign out = (state[D]);
```

```
endmodule
```

126. The following is the state transition table for a Moore state machine with one input, one output, and four states. Implement this state machine. Include an asynchronous reset that resets the FSM to state A.

State	Next state		Output
	in=0	in=1	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

Ans;

```
module top_module(
```

```
    input clk,
```

```
    input in,
```

```
    input areset,
```

```
    output out); //
```

```
    reg [2:0] state, next_state;
```

```
    parameter A = 1, B = 2, C = 3, D = 4;
```

```
    always @(*) begin
```

```
        case(state)
```

```
            A : next_state = (in == 1) ? B : A;
```

```
            B : next_state = (in == 1) ? B : C;
```

```
            C : next_state = (in == 1) ? D : A;
```

```
            D : next_state = (in == 1) ? B : C;
```

```
        endcase
```


```
    end
```

```
    always @(posedge clk or posedge areset) begin
```

```
        if(areset) state <= A;
```

```
        else state <= next_state;
```

```
    end
```

 

```
    assign out = (state == D);
```

```
endmodule
```

127. The following is the state transition table for a Moore state machine with one input, one output, and four states. Implement this state machine. Include a synchronous reset that resets the FSM to state A. (This is the same problem as Fsm3 but with a synchronous reset.)

State	Next state		Output
	in=0	in=1	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

Ans;

```
module top_module(
```

```
    input clk,
```

```
    input in,
```

```
    input reset,
```

```
    output out);
```

```
    reg [2:0] state, next_state;
```

```
    parameter A = 1, B = 2, C = 3, D = 4;
```

```
    always @(*) begin
```

```
        case(state)
```

```
            A : next_state = (in == 1) ? B : A;
```

```
            B : next_state = (in == 1) ? B : C;
```

```
            C : next_state = (in == 1) ? D : A;
```

```
            D : next_state = (in == 1) ? B : C;
```

```
        endcase
```

```
    end
```

```
    always @(posedge clk) begin
```


```
        if(reset) state <= A;
```

```
        else state <= next_state;
```

```
    end
```


```
    assign out = (state == D);
```

```
endmodule
```

 

128.

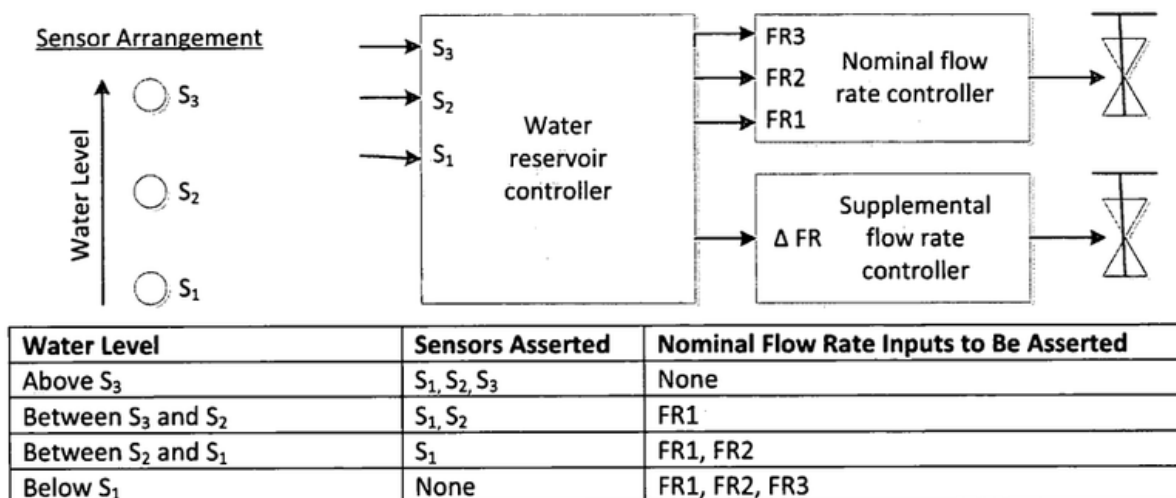Q4. [10] A large reservoir of water serves several users. In order to keep the level of water sufficiently high, three sensors are placed vertically at 5-inch intervals. When the water level is above the highest sensor (S_3), the input flow rate should be zero. When the level is below the lowest sensor (S_1), the flow rate should be at maximum (both Nominal flow valve and Supplemental flow valve opened). The flow rate when the level is between the upper and lower sensors is determined by two factors: the water level and the level previous to the last sensor change. Each water level has a nominal flow rate associated with it, as shown in the table below. If the sensor change indicates that the previous level was lower than the current level, the nominal flow rate should take place. If the previous level was higher than the current level, the flow rate should be increased by opening the Supplemental flow valve (controlled by ΔFR). Draw the Moore model state diagram for the water reservoir controller. Clearly indicate all state transitions and outputs for each state. The inputs to your FSM are S_1 , S_2 and S_3 ; the outputs are $FR1$, $FR2$, $FR3$ and ΔFR .



Ans;

module top_module (

input clk,

input reset,

input [3:1] s,

output fr3,

output fr2,

output fr1,

output dfr

);

localparam [2:0] A = 3'd0, //water level:below s1

B0 = 3'd1, //s1~s2, and previous level is higher

B1 = 3'd2, //s1~s2, and previous level is lower

C0 = 3'd3, //s2~s3, and previous level is higher

C1 = 3'd4, //s2~s3, and previous level is lower

D = 3'd5; //above s3

```
reg [2:0] state, next_state;
```

```
always @(posedge clk) begin
```

```
    if(reset) state <= A;
```

```
    else state <= next_state;
```

```
end
```

```
always @(*) begin
```

```
    case(state)
```

```
        A      :    next_state = (s[1]) ? B1 : A;
```

```
        B0     :    next_state = (s[2]) ? C1 : ((s[1]) ? B0 : A);
```

```
        B1     :    next_state = (s[2]) ? C1 : ((s[1]) ? B1 : A);
```

```
        C0     :    next_state = (s[3]) ? D  : ((s[2]) ? C0 : B0);
```

```
        C1     :    next_state = (s[3]) ? D  : ((s[2]) ? C1 : B0);
```

```
        D      :    next_state = (s[3]) ? D  : C0;
```

```
        default : next_state = 3'bxxx;
```

```
    endcase
```

```
end
```

```
always @(*) begin
```

```
    case(state)
```

```
        A : {fr3, fr2, fr1, dfr} = 4'b1111;
```

```
        B0 : {fr3, fr2, fr1, dfr} = 4'b0111;
```

```
        B1 : {fr3, fr2, fr1, dfr} = 4'b0110;
```

```
        C0 : {fr3, fr2, fr1, dfr} = 4'b0011;
```

```
        C1 : {fr3, fr2, fr1, dfr} = 4'b0010;
```

```
        D : {fr3, fr2, fr1, dfr} = 4'b0000;
```


```

        default : {fr3, fr2, fr1, dfr} = 4'bxxxx;
    endcase

end

endmodule


```

 

 129. The game Lemmings involves critters with fairly simple brains. So simple that we are going to model it using a finite state machine.

In the Lemmings' 2D world, Lemmings can be in one of two states: walking left or walking right. It will switch directions if it hits an obstacle. In particular, if a Lemming is bumped on the left, it will walk right. If it's bumped on the right, it will walk left. If it's bumped on both sides at the same time, it will still switch directions.

Implement a Moore state machine with two states, two inputs, and one output that models this behaviour.



Ans;

```

module top_module(
    input clk,
    input areset,

```



```

input bump_left,
input bump_right,
output walk_left,
output walk_right);


parameter LEFT = 0, RIGHT = 1;
reg state, next_state;
always @(*) begin
    case(state)
        LEFT : next_state = (bump_left) ? RIGHT : LEFT;
        RIGHT : next_state = (bump_right) ? LEFT : RIGHT;
    endcase
end

always @(posedge clk, posedge areset) begin
    if(areset) state <= LEFT;
    else begin
        state <= next_state;
    end
end

assign walk_left = (state == LEFT);
assign walk_right = (state == RIGHT);

```



endmodule

 

  130. In addition to walking left and right, Lemmings will fall (and presumably go "aaah!") if the ground disappears underneath them.

In addition to walking left and right and changing direction when bumped, when $\text{ground}=0$, the Lemming will fall and say "aaah!". When the ground reappears ($\text{ground}=1$), the Lemming will resume walking in the same direction as before the fall. Being bumped while falling does not affect the walking direction, and being bumped in the same cycle as ground disappears (but not yet falling), or when the ground reappears while still falling, also does not affect the walking direction.

Build a finite state machine that models this behaviour.



Ans;

```
module top_module(
    input clk,
    input areset,
    input bump_left,
    input bump_right,
    input ground,
    output walk_left,
    output walk_right,
    output aaah );

    localparam [1:0] WALK_L = 2'b00,
                    WALK_R = 2'b01,
```

```

        FALL_L = 2'b10,
        FALL_R = 2'b11;


    reg [1:0] state, next;

    always @(posedge clk or posedge areset) begin
        if(areset) state <= WALK_L;
        else begin
            state <= next;
        end
    end

    always @(*) begin
        case(state)
            WALK_L : next = (ground == 0) ? FALL_L : ((bump_left == 1) ? WALK_R
: WALK_L);
            WALK_R : next = (ground == 0) ? FALL_R : ((bump_right == 1) ?
WALK_L : WALK_R);
            FALL_L : next = (ground == 1) ? WALK_L : FALL_L;
            FALL_R : next = (ground == 1) ? WALK_R : FALL_R;
        endcase
    end

    assign walk_left = (state == WALK_L);
    assign walk_right = (state == WALK_R);
    assign aaah = ((state == FALL_L) || (state == FALL_R));
endmodule


```

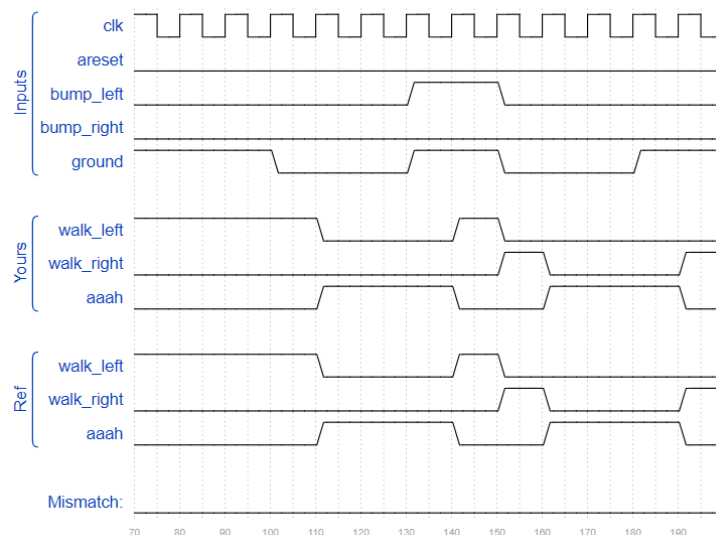

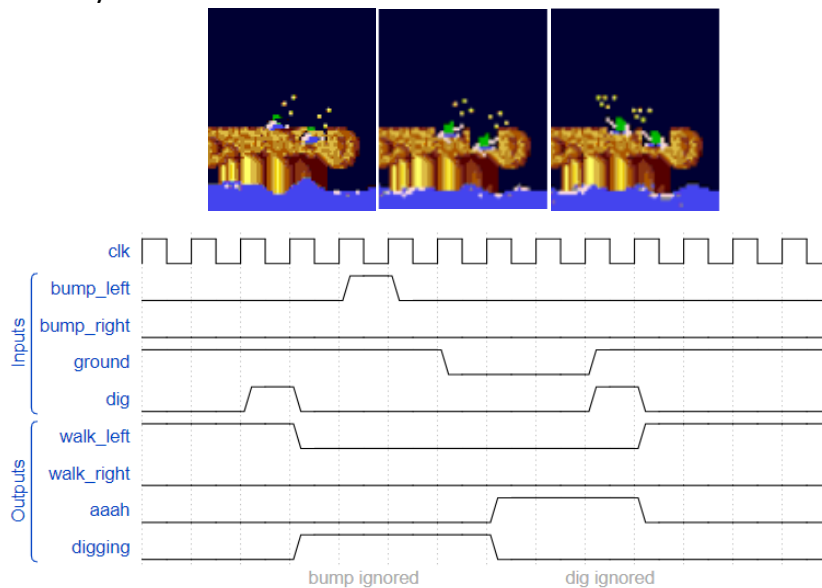131. In addition to walking and falling, Lemmings can sometimes be told to do useful things, like dig (it starts digging when dig=1). A Lemming can dig if it is currently walking on ground (ground=1 and not falling), and will continue digging until it reaches the other side (ground=0). At that point, since there is no ground, it will fall (aaah!), then continue walking in its original direction once it hits ground again. As with falling, being bumped while digging has no effect, and being told to dig when falling or when there is no ground is ignored.

(In other words, a walking Lemming can fall, dig, or switch directions. If more than one of these conditions are satisfied, fall has higher precedence than dig, which has higher precedence than switching directions.)

Extend your finite state machine to model this behaviour.



Ans;

```
module top_module(
```

```
    input clk,
```

```
    input areset,
```

```
    input bump_left,
```

```
    input bump_right,
```

```
    input ground,
```


```
    input dig,
```

```
    output walk_left,
```

```
    output walk_right,
```

```
    output aaah,
```

```
    output digging );
```

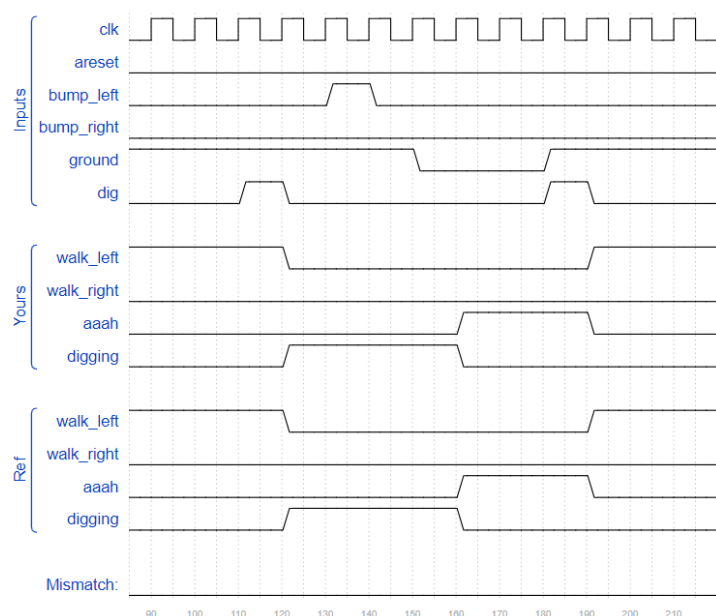

```

localparam [2:0] WALK_L = 3'b000,
                WALK_R = 3'b001,
                FALL_L = 3'b010,
                FALL_R = 3'b011,
                DIG_L  = 3'b100,
                DIG_R  = 3'b101;

reg[2:0] state,next;

always@(posedge clk or posedge areset)begin
    if(areset) state <= WALK_L;
    else state<=next;
end

always @(*) begin
    case(state)
        WALK_L : begin
            if(!ground) next = FALL_L;
            else begin
                if(dig) next = DIG_L;
                else begin
                    if(bump_left) next = WALK_R;
                    else next = WALK_L;
                end
            end
        end
        WALK_R : begin
            if(!ground) next = FALL_R;
            else begin
                if(dig) next = DIG_R;
                else begin

```

```

        if(bump_right) next = WALK_L;
        else next = WALK_R;
    end
end
end

FALL_L : next = (ground) ? WALK_L : FALL_L;
FALL_R : next = (ground) ? WALK_R : FALL_R;
DIG_L : next = (ground) ? DIG_L : FALL_L;
DIG_R : next = (ground) ? DIG_R : FALL_R;
endcase
end



assign walk_left = (state == WALK_L);
assign walk_right = (state == WALK_R);
assign aaah = ((state == FALL_L) || (state == FALL_R));
assign digging = ((state == DIG_L) || (state == DIG_R));
endmodule

```


132. Although Lemmings can walk, fall, and dig, Lemmings aren't invulnerable. If a Lemming falls for too long then hits the ground, it can splatter. In particular, if a Lemming falls for more than 20 clock cycles then hits the ground, it will splatter and cease walking, falling, or digging (all 4 outputs become 0), forever (Or until the FSM gets reset). There is no upper limit on how far a Lemming can fall before hitting the ground. Lemmings only splatter when hitting the ground; they do not splatter in mid-air.

Extend your finite state machine to model this behaviour.

Falling for 20 cycles is survivable:

  

Falling for 21 cycles causes splatter:

 

Ans;

```
module top_module(
    input clk,
    input areset, // Freshly brainwashed Lemmings walk left.
    input bump_left,
    input bump_right,
    input ground,
    input dig,
    output walk_left,
    output walk_right,
    output aaah,
    output digging );

    localparam [2:0] WALK_L = 3'b000,
                     WALK_R = 3'b001,
                     FALL_L = 3'b010,
                     FALL_R = 3'b011,
                     DIG_L = 3'b100,
                     DIG_R = 3'b101,
                     SPLATTER = 3'b110;

    reg [2:0] state, next;
    reg [6:0] count;

    always @(posedge clk or posedge areset) begin
```

```

if(areset) state <= WALK_L;
else if(state == FALL_R || state == FALL_L) begin
    count <= count + 1;
    state <= next;
end
else begin
    state <= next;
    count <= 0;
end
end
always @(*) begin
    case(state)
        WALK_L : begin
            if(!ground) next = FALL_L;
            else begin
                if(dig) next = DIG_L;
                else begin
                    if(bump_left) next = WALK_R;
                    else next = WALK_L;
                end
            end
        end
        WALK_R : begin
            if(!ground) next = FALL_R;
            else begin
                if(dig) next = DIG_R;
                else begin
                    if(bump_right) next = WALK_L;
                    else next = WALK_R;
                end
            end
        end
    endcase
end

```



```

        end

    end

end

FALL_L : begin

    if(ground) begin

        if(count > 19) next = SPLATTER;

        else next = WALK_L;

    end

    else next = FALL_L;

end

FALL_R : begin

    if(ground) beg

        if(count > 19)

            else next = \

        end

        else next = FA

    end

    DIG_L : next = (

    DIG_R : next = (

        SPLATTER : next = SPLATTER;

    endcase

end

assign walk_left = (state == WALK_L);


assign walk_right = (state == WALK_R);

assign aaah = ((state == FALL_L) || (state == FALL_R));


assign digging = ((state == DIG_L) || (state == DIG_R));

endmodule

```

 

 133. Given the following state machine with 1 input and 2 outputs:



Suppose this state machine uses one-hot encoding, where state[0] through state[9] correspond to the states S0 through S9, respectively. The outputs are zero unless otherwise specified.

Implement the state transition logic and output logic portions of the state machine (but not the state flip-flops). You are given the current state in state[9:0] and must produce next_state[9:0] and the two outputs. Derive the logic equations by inspection assuming a one-hot encoding. (The testbench will test with non-one hot inputs to make sure you're not trying to do something more complicated).

Ans;

```
module top_module(
```

```
    input in,
```

```
    input [9:0] state,
```

```
    output [9:0] next_state,
```

```
    output out1,
```

```
    output out2);
```

```
    localparam S0 = 0, S1 = 1, S2 = 2, S3 = 3, S4 = 4,
```

```
               S5 = 5, S6 = 6, S7 = 7, S8 = 8, S9 = 9;
```

```
    //states
```

```
    assign next_state[S0] = (state[S0] & !in) | (state[S1] & !in) | (state[S2] & !in) |
    (state[S3] & !in) |
```

```
                (state[S4] & !in) | (state[S7] & !in) |
```

```
    (state[S8] & !in) | (state[S9] & !in);
```

```
    assign next_state[S1] = (state[S0] & in) | (state[S8] & in) | (state[S9] & in);
```

```

assign next_state[S2] = state[S1] & in;

assign next_state[S3] = state[S2] & in;

assign next_state[S4] = state[S3] & in;

assign next_state[S5] = state[S4] & in;

assign next_state[S6] = state[S5] & in;

assign next_state[S7] = (state[S6] & in) | (state[S7] & in);

assign next_state[S8] = state[S5] & !in;

assign next_state[S9] = state[S6] & !in;


//output

assign out1 = state[S8] | state[S9];

assign out2 = state[S7] | state[S9];

```

endmodule

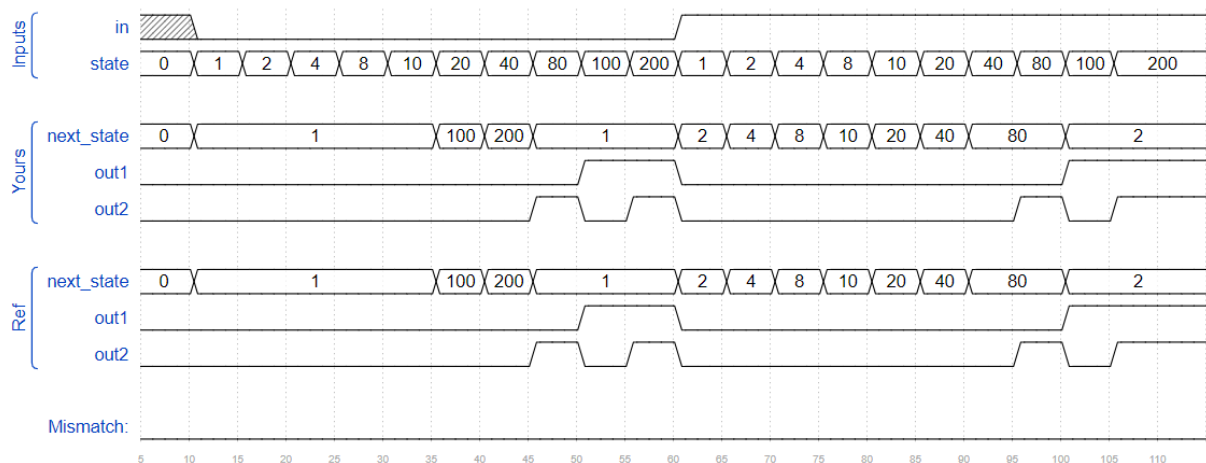

134. The PS/2 mouse protocol sends messages that are three bytes long. However, within a continuous byte stream, it's not obvious where messages start and end. The only indication is that the first byte of each three byte message always has bit[3]=1 (but bit[3] of the other two bytes may be 1 or 0 depending on data).

We want a finite state machine that will search for message boundaries when given an input byte stream. The algorithm we'll use is to discard bytes until we see one with bit[3]=1. We then assume that this is byte 1 of a message, and signal the receipt of a message once all 3 bytes have been received (done).

The FSM should signal done in the cycle immediately after the third byte of each message was successfully received.

Ans;

```
module top_module(
    input clk,
    input [7:0] in,
    input reset, // Synchronous reset
    output done); //

    localparam [1:0] BYTE1 = 2'b00,
                    BYTE2 = 2'b01,
                    BYTE3 = 2'b10,
                    DONE  = 2'b11;

    reg [1:0] state, next;

    // State transition logic (combinational)
    always @(*) begin
        case(state)
            BYTE1 : next = (in[3]) ? BYTE2 : BYTE1;
            BYTE2 : next = BYTE3;
            BYTE3 : next = DONE;
            DONE  : next = (in[3]) ? BYTE2 : BYTE1;
        endcase
    end

    // State flip-flops (sequential)
    always @(posedge clk) begin
        if(reset) state <= BYTE1;
        else state <= next;
    end
end
```

```
// Output logic


assign done = (state == DONE);

endmodule
```

135. Now that you have a state machine that will identify three-byte messages in a PS/2 byte stream, add a datapath that will also output the 24-bit (3 byte) message whenever a packet is received (out_bytes[23:16] is the first byte, out_bytes[15:8] is the second byte, etc.).

out_bytes needs to be valid whenever the done signal is asserted. You may output anything at other times (i.e., don't-care).

For example:

 

Ans;

```
module top_module(
    input clk,
    input [7:0] in,
    input reset, // Synchronous reset
    output [23:0] out_bytes,
    output done); //

    localparam [1:0] BYTE1 = 2'b00,
                    BYTE2 = 2'b01,
                    BYTE3 = 2'b10,
                    DONE = 2'b11;

    reg [1:0] state, next;
```

```

reg [23:0] data;

// State transition logic (combinational)
always @(*) begin
    case(state)
        BYTE1 : next = (in[3]) ? BYTE2 : BYTE1;
        BYTE2 : next = BYTE3;
        BYTE3 : next = DONE;
        DONE  : next = (in[3]) ? BYTE2 : BYTE1;
    endcase
end

// State flip-flops (sequential)
always @(posedge clk) begin
    if(reset) state <= BYTE1;
    else state <= next;
end

// New: Datapath to store incoming bytes.
always @(posedge clk) begin
    if (reset) data <= 24'b0;
    else data <= {data[15:8], data[7:0], in};
end


// Output logic
assign done = (state == DONE);
assign out_bytes = (done) ? data : 23'b0;
endmodule

```


136. In many (older) serial communications protocols, each data byte is sent along with a start bit and a stop bit, to help the receiver delimit bytes from the stream of bits. One common scheme is to use one start bit (0), 8 data bits, and 1 stop bit (1). The line is also at logic 1 when nothing is being transmitted (idle).

Design a finite state machine that will identify when bytes have been correctly received when given a stream of bits. It needs to identify the start bit, wait for all 8 data bits, then verify that the stop bit was correct. If the stop bit does not appear when expected, the FSM must wait until it finds a stop bit before attempting to receive the next byte.

Error-free:

 

 Stop bit not found. First byte is discarded:



Ans;

```
module top_module(
```

```
    input clk,
```

```
    input in,
```

```
    input reset, // Synchronous reset
```

```
    output done
```

```
);
```

```
    localparam [2:0] IDLE = 3'b000,
```

```
                    START = 3'b001,
```

```
                    RECEIVE = 3'b010,
```

```
                    WAIT = 3'b011,
```

```
STOP = 3'b100;
```

```
reg [2:0] state, next;
```

```
reg [3:0] i;
```

```
always @(*) begin
```

```
    case(state)
```

```
        IDLE : next = (in) ? IDLE : START;
```

```
        START : next = RECEIVE;
```

```
        RECEIVE : begin
```

```
            if (i == 8) begin
```

```
                if (in) next = STOP;
```

```
                else next = WAIT;
```

```
            end
```

```
            else next = RECEIVE;
```

```
        end
```

```
        WAIT : next = (in) ? IDLE : WAIT;
```

```
        STOP : next = (in) ? IDLE : START;
```

```
    endcase
```

```
end
```

```
always @(posedge clk) begin
```

```
    if(reset) state <= IDLE;
```

```
    else state <= next;
```

```
end
```

```
always @(posedge clk) begin
```

```
    if (reset) begin
```

```
        done <= 0;
```

```
        i <= 0;
```

```
    end
```



```

else begin
    case(next)
        RECEIVE : begin
            done <= 0;
            i = i + 1;
        end
        STOP : begin
            done <= 1;
            i <= 0;
        end
        default : begin
            done <= 0;
            i <= 0;
        end
    endcase
end

end


endmodule

```

137. Now that you have a finite state machine that can identify when bytes are correctly received in a serial bitstream, add a datapath that will output the correctly-received data byte. `out_byte` needs to be valid when `done` is 1, and is don't-care otherwise.

Note that the serial protocol sends the least significant bit first.

Error-free:

 

Ans;

```

module top_module(
    input clk,
    input in,
    input reset, // Synchronous reset
    output [7:0] out_byte,
    output done
);

// Use FSM from Fsm_serial
localparam [2:0] IDLE      = 3'b000,
                START      = 3'b001,
                RECEIVE = 3'b010,
                WAIT  = 3'b011,
                STOP   = 3'b100;

    reg [2:0] state, next;
    reg [3:0] i;
    reg [7:0] out;

    always @(*) begin
        case(state)
            IDLE : next = (in) ? IDLE : START;
            START : next = RECEIVE;
            RECEIVE : begin
                if (i == 8) begin
                    if (in) next = STOP;
                    else next = WAIT;
                end
                else next = RECEIVE;
            end
        endcase
    end

```

```

        end

        WAIT : next = (in) ? IDLE : WAIT;

        STOP : next = (in) ? IDLE : START;

    endcase

end

```

```

always @(posedge clk) begin

    if(reset) state <= IDLE;

    else state <= next;

end

```

```

always @(posedge clk) begin

    if (reset) begin

        done <= 0;

        i <= 0;

    end

    else begin

        case(next)

            RECEIVE : begin

                done <= 0;

                i = i + 1;

            end

            STOP : begin

                done <= 1;

                i <= 0;

            end

            default : begin

                done <= 0;

                i <= 0;

            end

        endcase

    end

end

```

```

                                end
                                endcase
                                end
                                end

                                // New: Datapath to latch input bits.
                                always @(posedge clk) begin
                                    if (reset) out <= 0;
                                    else if (next == RECEIVE)
                                        out[i] <= in;

                                end

                                assign out_byte = (done) ? out : 8'b0;
endmodule

```

139. Create a finite state machine to recognize these three sequences:

0111110: Signal a bit needs to be discarded (disc).

01111110: Flag the beginning/end of a frame (flag).


01111111...: Error (7 or more 1s) (err).

When the FSM is reset, it should be in a state that behaves as though the previous input were 0.


Here are some example sequences that illustrate the desired operation.

Discard 0111110:


Discard 0111110:

 

Flag 01111110:

 

 Reset behaviour and error 01111111 . . . :



Ans;

```
module top_module(
```

```
    input clk,
```

```
    input reset, // Synchronous reset
```

```
    input in,
```

```
    output disc,
```

```
    output flag,
```

```
    output err);
```

```
    localparam [3:0] NONE = 0,
```

```
                ONE = 1,
```

```
                TWO = 2,
```

```
                THREE = 3,
```

```
                FOUR = 4,
```

```
                FIVE = 5,
```

```
                SIX = 6,
```

```
                DISC = 7,
```

```
                FLAG = 8,
```

```
                ERR = 9;
```

```
    reg [3:0] state, next;
```

```
    always @(*) begin
```

```

    case (state)
        NONE : next = (in) ? ONE  : NONE;
        ONE   : next = (in) ? TWO   : NONE;
        TWO   : next = (in) ? THREE : NONE;
        THREE : next = (in) ? FOUR  : NONE;
        FOUR  : next = (in) ? FIVE  : NONE;
        FIVE  : next = (in) ? SIX   : DISC;
        SIX   : next = (in) ? ERR   : FLAG;
        DISC  : next = (in) ? ONE   : NONE;
        FLAG  : next = (in) ? ONE   : NONE;
        ERR   : next = (in) ? ERR   : NONE;
    endcase
end

always @(posedge clk) begin
    if (reset)
        state <= NONE;
    else
        state <= next;
    end

    assign disc = (state == DISC);
    assign flag = (state == FLAG);
    assign err  = (state == ERR);
endmodule

```

140. Implement a Mealy-type finite state machine that recognizes the sequence "101" on an input signal named x. Your FSM should have an output signal, z, that is asserted to logic-1 when the "101" sequence is detected. Your FSM should also have an active-low asynchronous reset. You may only have 3 states in your state machine. Your FSM should recognize overlapping sequences.

Ans;

```
module top_module (  
    input clk,  
    input aresetn, // Asynchronous active-low reset  
    input x,  
    output z );  
  
    localparam [1:0] IDLE    = 0,  
                    ONE      = 1,  
                    ONE_ZERO = 2;  
  
    reg [1:0] state, next;  
  
    always @(*) begin  
        case (state)  
            IDLE : begin  
                next = (x) ? ONE : IDLE;  
                z = 0;  
            end  
            ONE : begin  
                next = (x) ? ONE : ONE_ZERO;  
                z = 0;  
            end  
            ONE_ZERO : begin  
                if (x) begin  
                    next = ONE;  
                    z = 1;  
                end  
                else begin
```

```

        next = IDLE;
        z = 0;
    end
end
endcase
end

always @(posedge clk or negedge aresetn) begin
    if (~aresetn) state <= IDLE;
    else state <= next;

end
endmodule

```

